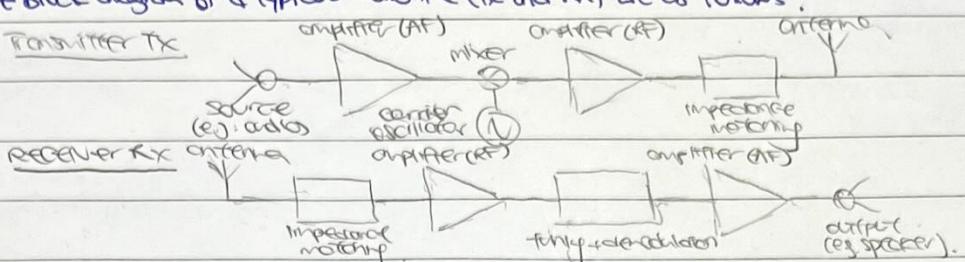


**Radio****Radio**

- Radio uses a carrier wave (high freq. signal) which is modulated by an information signal (audio/digital data).

Common modulation schemes include AM, FM, PSK.


- The block diagram of a typical radio link (Tx and Rx) are as follows.



- To allow efficient use of the EM spectrum, channels are allocated w/ special carrier freq. and BW for diff. applications.

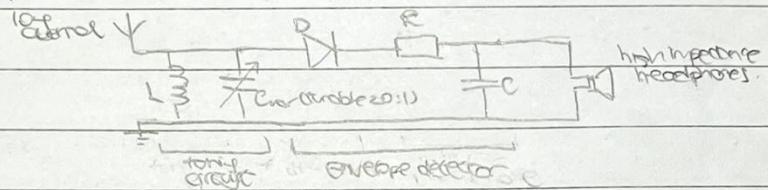**crystal set receiver.**

- The circuit for the crystal set receiver is as follows:



- The radio station is selected by tuning the LC resonant circuit to the right freq., where an AC voltage appears (w/ AM) across them. The envelope (desired audio signal) is then retrieved using the diode LIF.

- This arrangement has the following drawbacks

↳ Low power o/p : No gain  $\rightarrow$  only a fraction of RF power is available as audio o/p.


↳ Limited tuning range : Chir varifer 20:1  $\rightarrow$  f varifer  $\approx$  20:1.

↳ Low selectivity : Low Q  $\rightarrow$  can hear neighbouring freq.

↳ BW varies w/ freq :  $B = \frac{f_0}{Q}$   $\rightarrow$  depends on  $f_0$ .

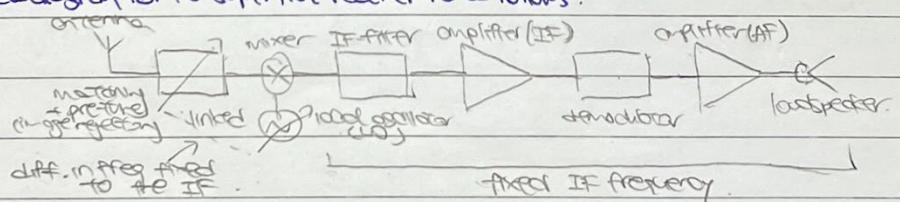**Superheterodyne receiver (Super HET)**

- The block diagram for the superhet receiver is as follows:




- The mixer "moves" the selected carrier freq. down to a fixed IF of which the rest of the circuit operates.

$\rightarrow$  gain and BW of the downstream circuitry is const. regardless of the freq. to which the local oscillator is tuned to.

### Field effect transistors (FET)
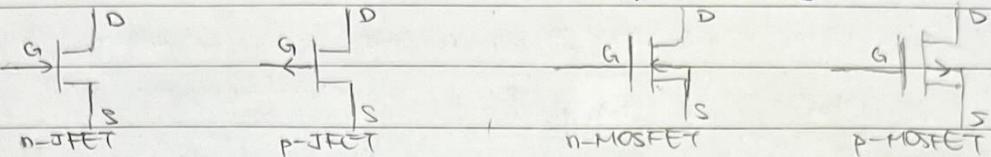
#### Field effect transistors (FET)

- FETs are voltage-controlled devices, where the field from the gate influences the passage of charge carriers along a channel b/w source and drain.
- There are two types of FETs: JFET and MOSFET
  - ↳ JFET: Gate is a reverse-biased junction in normal op's and negligible gate current flows.
  - ↳ MOSFET: Gate is isolated by a thin insulation layer and no gate current flows.



#### FET characteristics

- When  $V_{GS}$  rises above a threshold offset voltage  $V_{th}$ , then the transistor begins to conduct a current  $I_{DS}$  b/w the drain and source, w/ voltage  $V_{DS}$  across it.

- There are three regimes of interest:

↳ 1)  $V_{GS} - V_{th} < 0$  ;  $I_{DS} = 0$

↳ 2)  $V_{GS} - V_{th} \geq V_{DS}$  ;  $I_{DS} = 2K[(V_{GS} - V_{th})V_{DS} - \frac{V_{DS}^2}{2}]$

↳ 3)  $V_{GS} - V_{th} \leq V_{DS}$  ;  $I_{DS} = K(V_{GS} - V_{th})^2$


(Note ③ is just ② but  $V_{DS} = V_{GS} - V_{th}$ )

where  $K = -\frac{C_{MFEW}}{2L}$

[Device is off]

[Voltage-controlled resistor (linear)]

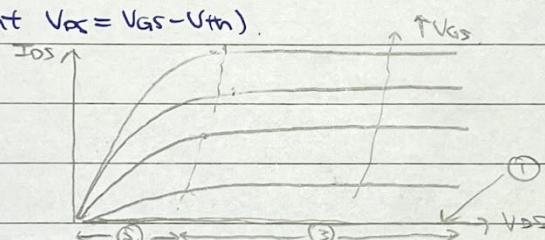[Voltage-controlled current source (saturation)]



- The FET therefore has a no. of characteristics and applications which differ from BJTs:

↳ High i/p impedance  $Z_{in}$

↳ Used as electrically-programmed variable resistor


↳ can be used w/  $V_{DS} \approx 0$  → switch

↳ Voltage gain inferior to BJT.

\* The IGBT has the i/p characteristics of a FET and o/p characteristics of a BJT → speed for medium speed (nms) and high power switching.

Small signal model [saturation regime,  $V_{GS} - V_{th} \leq V_{DS}$ ].

- The FET can be modelled using the DSM.

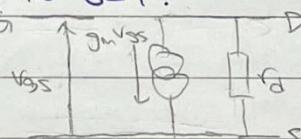


- The FET is not normally used as a plain amplifier as its gain is less than a BJT w/ similar  $I_{DS}$ . However, it has almost infinite i/p impedance  $Z_{in}$ , → ideal i/p stage for an amplifier which does not load the circuit it is connected to (pH probes, bio-potential probe).
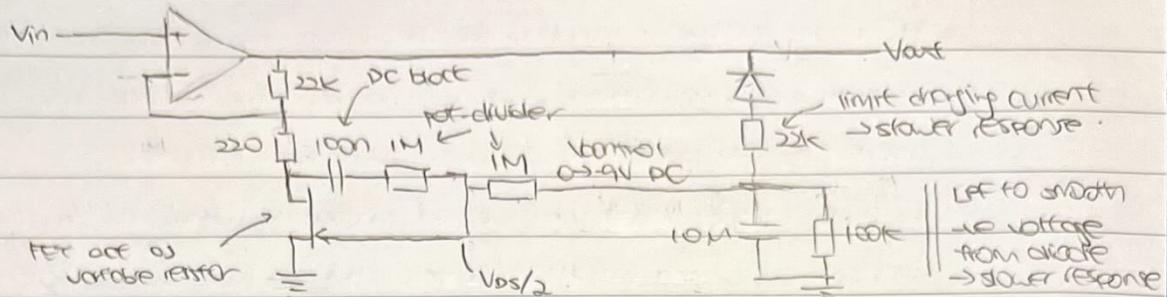
# For Personal Use Only -bkwk2

Voltage-controlled attenuator [linear regime,  $V_{GS} - V_{TH} \geq V_{DS}$ ]

- The circuit for a voltage-controlled attenuator is as follows:




- The FET is in the linear regime and acts as a variable resistor

$$V_{GS} - V_{TH} \geq V_{DS} : R_{DS} = \frac{V_{GS}}{I_{DS}} = \frac{1}{2k[(V_{GS} - V_{TH}) - \frac{V_{DS}}{2}]} \quad \text{small non-linearity}$$


- The 1MΩ resistors act as potential dividers to introduce an additional  $\frac{V_{DS}}{2}$  at the gate to remove the nonlinearity of the FET, 100nF capacitor acts as a DC block.
- $V_{control}$  is linked to the op-amp via a LPF.  $\uparrow|V_{out}| \rightarrow \downarrow V_{control} \rightarrow \downarrow V_{GS} - V_{TH} \rightarrow \uparrow R_{DS} \rightarrow \downarrow \text{Gain}$
- The LPF smooths/averages -ve voltage from diode so  $V_{control}$  does not change too quickly and alter the gain within an audio cycle (and distort the waveform).

Sample and hold circuit [linear regime,  $V_{GS} - V_{TH} \geq V_{DS}$ ]

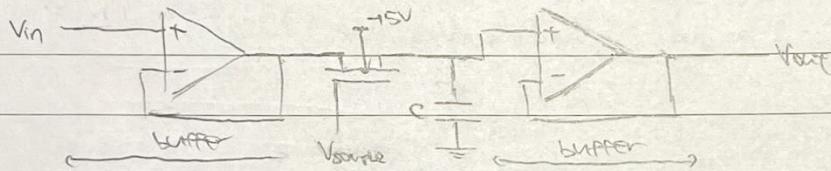- The circuit for the sample and hold (analog switch) circuit is as follows:



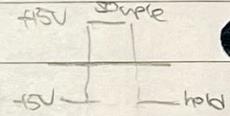- The FET is in the linear regime and acts as an analog switch
- When  $V_{sample}$  is HIGH, the switch is closed  $\rightarrow V_{out} = V_{in}$
- When  $V_{sample}$  is LOW, the switch is open  $\rightarrow V_{out}$  freezed by capacitor.
- Setting substrate connection to the most -ve potential prevents parasitic latch-up on IC devices.



Interfacing between logic signals and high power load

- For heavy power switching, the MOSFET offers a simple interface b/w TTL and high power load

TTL current draw (MOSFET has logic C) TTL (5V device)	10mA 20mA 10A 2kW load
---	---------------------------------

=D-TE


- The FET is in the linear regime and acts as an analog switch
- Note power MOSFETs have large gate capacitance. (High  $C_{GS}$  and Miller effect on  $C_{GD}$ )
- $\sim 100\text{ pF} \rightarrow$  rapid switching from TTL not viable  $\rightarrow$  we would req. specialized IC drivers.

# For Personal Use Only -bkwk2

## Bipolar junction transistors (BJT)
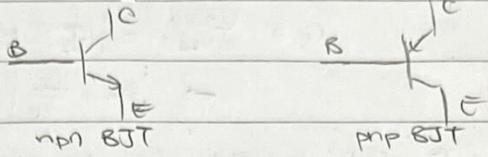
### Bipolar junction transistors (BJT)

- BJTs are current-controlled devices - where the current at the base influences the passage of charge carriers between emitter and collector.



The Ebers-Moll model.

- We can model the BJT using the Ebers-Moll model.

$$I_C = I_S \left[ \exp\left(\frac{qV_{BE}}{kT}\right) - 1 \right] \approx I_S \exp\left(\frac{V_{BE}}{V_T}\right)$$

where  $I_S$  is the saturation current (determined by transistor construction)

and  $V_T$  is the thermal voltage, given by  $V_T = \frac{kT}{q}$  ( $kT = 25 \text{ mV}$  at room temp.)

- This is similar in form to the pn diode eqn. For the base-emitter diode,

$$I_B = I_S' \left[ \exp\left(\frac{qV_{BE}}{kT}\right) - 1 \right] \approx I_S' \exp\left(\frac{V_{BE}}{V_T}\right)$$

- therefore the current gain of the transistor  $h_{FE} = \frac{I_C}{I_B} = \frac{I_S'}{I_S}$  is roughly const. (over a limited range).


$h_{FE}$  is often  $\sim 100-500$  for low current, small signal devices.

- The current gain  $h_{FE}$  increases as temp.  $T$  increases (cannot tell from Ebers-Moll since both  $I_S$  and  $V_T$  depend on temp.  $T$ )


- Due to the exponential nature of Ebers-Moll, a small  $\Delta V_{BE}$  can result in large  $\Delta I_C$  (at room temp.  $\Delta V_{BE}$  by  $60 \text{ mV} \rightarrow \Delta I_C \times 10$ ).

## Small signal model

- The BJT can be modelled using the SSM.

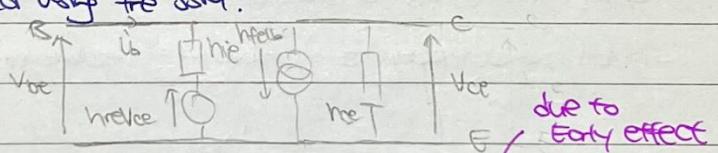

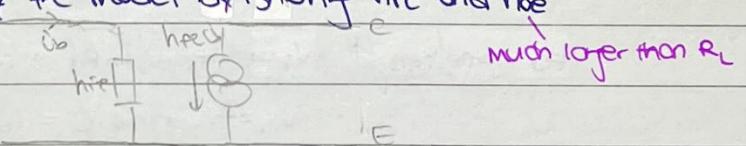and we would often simplify the model by ignoring  $h_{re}$  and  $h_{oe}$



- \* The simplified model only results in a few % error  $\rightarrow$  okay in most cases.

↳ e.g. For BC108 @  $I_C=2 \text{ mA}$ ,  $V_{CE}=5 \text{ V}$ ,  $h_{FE}=300$ ,  $h_{ie}=3 \times 10^3 \Omega$ ,  $h_{re}=2 \times 10^4$ ,  $h_{oe}=[4 \times 10^4 \Omega]^2$

consider the case  $V_{CC}=10 \text{ V}$ ,  $R_L=2500 \Omega$ ,  $V_{BE}=1 \text{ V}$

$$\text{Ignore } h_{oe}: R = 2.5 \text{ k}\Omega, R = \frac{2.5k-2.5k}{2.5k+40k} = 2.353 \text{ k}\Omega. \text{ so } \%R = \frac{2.5k-2.353k}{2.5k} = 5.7\%.$$

$$\text{Ignore } h_{re}: V_{oehre} = 0.2 \text{ mV}, V_{be} = i_B h_{re} \approx \frac{i_e}{h_{fe}} h_{re} = \frac{V_{be}}{R_L} h_{re} = 4 \text{ mV}$$

$$\text{so } \%V_{be} = \frac{0.2 \text{ mV}}{2 \text{ mA}} = 5\%.$$

# For Personal Use Only -bkwk2

## Emitter resistance model

- The emitter resistance  $r_e$  is defined as


$$r_e = \frac{\Delta V_{BE}}{\Delta I_C} \approx \frac{\Delta V_{BE}}{\Delta I_C}$$

- From Ebers Moll eqn,  $I_C = I_s [\exp(\frac{V_{BE}}{V_t}) - 1] \approx I_s \exp(\frac{V_{BE}}{V_t})$ , we have

$$r_e = \left( \frac{dI_C}{dV_{BE}} \right)^{-1} = \left[ \frac{1}{V_t} I_s \exp\left(\frac{V_{BE}}{V_t}\right) \right]^{-1} = \frac{V_t}{I_C}$$

$$\rightarrow r_e = \frac{V_t}{I_C}$$

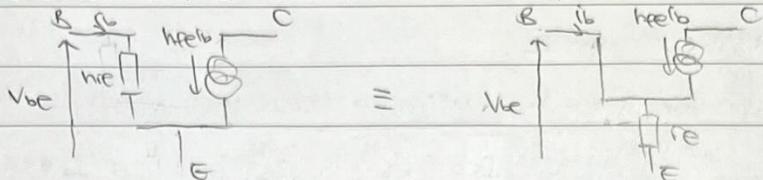- The emitter resistance model is equivalent to the input impedance model.



For equivalence of  $V_{BE}$ , we req.  $V_{BE}$  and  $I_C$  to match in the two models.

$$V_{BE} = i_b h_{ie} = h_{FE} i_b r_e$$


$$\rightarrow r_e = \frac{h_{ie}}{h_{FE}}$$

- Analysis for  $Z_{in}$  easier using  $h_{ie}$  model ; Analysis for  $Z_{out}$  easier using  $r_e$  model.

## Simple bipolar transistor amplifier design
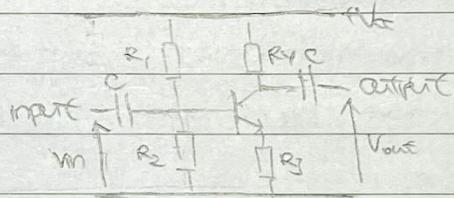
### Standard amplifier circuit.

- The standard amplifier circuit is as follows:




↳  $C_1$  are coupling capacitors (DC block)

↳  $R_1, R_2$  provide DC base bias current

↳  $R_3$  gives -ve FB to stabilise bias pt.

↳  $R_4$  allows for opf voltage swing

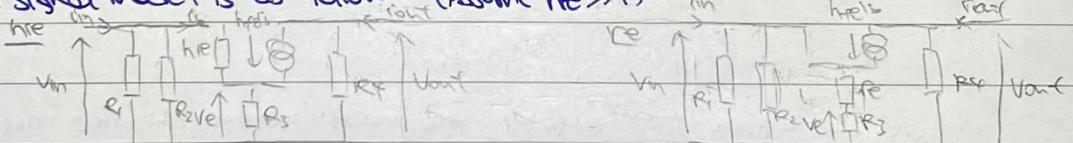- Small signal model is as follows: (assume  $h_{FE} \gg 1$ )



At the input,

$$V_E = (1 + h_{FE}) i_b R_3 = h_{FE} i_b R_3$$

$$V_{in} = V_E + h_{ie} i_b = i_b (h_{FE} R_3 + h_{ie})$$

$$\boxed{\frac{V_E}{V_{in}} = \frac{R_3}{R_3 + r_e}}$$

$$R_{in} = R_1 // R_2 // \frac{V_{in}}{i_b} = R_1 // R_2 // (h_{FE} R_3 + h_{ie}) = R_1 // R_2 // h_{FE} (R_3 + r_e)$$

At the output,

$$V_{out} = -(h_{FE} i_b - i_{out}) R_4 = -\frac{h_{FE} R_4 V_{in}}{h_{FE} R_3 + h_{ie}} + R_4 i_{out}$$

$$Gain = \frac{V_{out}}{V_{in}} = -\frac{h_{FE} R_4}{h_{FE} R_3 + h_{ie}} = -\frac{R_4}{R_3 + r_e}$$

$$R_{out} = \frac{V_{out}}{i_{out}} = R_4$$

$$\Rightarrow \boxed{Gain = -\frac{R_4}{R_3 + r_e}}, \boxed{R_{in} = R_1 // R_2 // h_{FE} (R_3 + r_e)}, \boxed{R_{out} = R_4}, \boxed{\frac{V_E}{V_{in}} = \frac{R_3}{R_3 + r_e}}$$

# For Personal Use Only -bkwk2

Designing a multi-stage bipolar transistor amplifier.

① Selecting the no. of stages, gain and ip/dlp impedances.

- The required power gain (in dB) is given by

$$\text{Power gain (dB)} = 10 \log_{10} \left( \frac{P_{out}}{P_{in}} \right)$$

- Assuming each transistor stage gives a gain of 20dB, we can find the no. of transistor stages, N

$$N = \frac{\text{Power gain (dB)}}{20}$$

- We round N to the nearest integer.

- The no. of couplings b/w the source and load is given by N+1. Assuming the ip and dlp impedances are matched, we lose 50% of the signal voltage of each coupling.

$$\text{Total gain product} = \frac{V_{out}}{V_{in}} \times \frac{1}{(0.5)^{N+1}}$$

if  $R_{in} \neq R_{out} \rightarrow$  coupling loss  $\neq 50\%$   
then find via potential divider.

Therefore the req. voltage gain at each transistor stage is given by .

$$\text{Voltage gain per stage} = (\text{Total gain product})^{\frac{1}{N}}$$

+ The voltage gain calculated is the min. gain  $\rightarrow$  usually  $\times 1.2$  to have a margin.

- We choose the ip and dlp impedance of each stage s.t. the source/load impedances are blended across the N transistor stages.

$$\frac{R_{out}}{R_{in}} = \left( \frac{\text{Load}}{\text{Source}} \right)^{\frac{1}{N}}$$

+ Note  $R_{in(1)} = \text{Source}$  and  $R_{out(N)} = \text{Load}$ .

② Selecting resistor values.

- Consider the following rules of thumb for steady DC voltages req. on the transistors for correct biasing,

$$V_C = \frac{V_{CC}}{2} \quad V_E \approx \frac{V_{CC}}{20} \quad V_B = (V_E + 0.7) \times 1.2$$

Recall for the standard amplifier circuit (one stage), and assume that  $R_2 \gg r_e$  ↗ shorting  $r_e$  is okay, even for the high current stage.

$$\text{Gain} = -\frac{R_4}{R_2 + r_e} \approx -\frac{R_4}{R_2} \quad R_{in} = R_1 // R_2 // h_{FE}(R_{load}) \approx R_1 // R_2 // h_{FE} \quad R_{out} = R_4.$$

(i) Find  $R_{in}$  and  $R_{out}$  for each stage using the ratio  $\frac{R_{out}}{R_{in}}$  found above +  $R_{in(1)} = \text{Source}/R_{out(N)} = \text{Load}$ .

(ii) Use  $R_{out} = R_4$  to find  $R_4$

(iii) Use Gain =  $-\frac{R_4}{R_2}$  to find  $R_2$

(iv) Use  $R_2 = 15 - 2 \times R_{in}$  to find  $R_2$  (rule of thumb)

(v) Use  $V_B = \frac{R_2}{R_2 + R_1} V_{CC}$  to find  $R_1$ , where  $V_B = (V_E + 0.7) \times 1.2$  and  $V_E \approx \frac{V_{CC}}{20}$ ,

+ If  $V_{CC}$  is not given, then

(i) calculate the dlp voltage swing using  $V_o = I_{max} R_{load}$

(ii) We req.  $V_{CC}$  at least  $2 \times V_o$  to avoid clipping  $\rightarrow$  choose  $V_{CC} = 4 \times V_o$  to introduce a safety factor of 2

+ If  $I_C$  is too low (mA), reduce  $R_4$  to get a more stable bias pt. ↗ be careful w/ calculating the req. voltage gain as coupling loss  $\neq 50\%$ .

+ For multi-stage amplifier, we can simply divide the  $R_1-R_2$  values by the  $\frac{R_{out}}{R_{in}}$  ratio to avoid recalculating for each stage.

# For Personal Use Only -bkwk2

## ② selecting capacitor values.

- The series capacitors for AC signal coupling between stages are selected in combination w/ the  $V_{IF}$  and  $A_{IF}$  impedances to give a low freq. response roll-off.

$$f_{3dB} = \frac{1}{2\pi(R_{in}(n) + R_{in}(n+1)C)}$$

formula for coupling circuit  
w/ low freq. response roll-off  
(high-pass). in textbook.

- \* Note for audio applications, we typically choose  $f_{3dB} = 20\text{ Hz}$ . If the amplifier circuit is req. to operate down to  $f_{low}$ , we choose  $f_{3dB} = 0.5 \times f_{low}$

- \* For multi-stage amplifier, w/ resistor values, we can simply scale using the  $\frac{R_{out}}{R_{in}}$  ratio.

## ③ selecting the transistor.

- We choose the highest hFE device available which can handle the collector current  $I_C$ , supply voltage  $V_{CC}$  and power dissipation  $I_C \cdot \frac{V_{CC}}{2}$ , all w/ a safety margin of 50%.

- \* For triodes, hFE is usually given and we do not need to select the transistor.

## ④ check the effect of low hFE, particularly for the high current stage.

- For the high current stage, the transistor hFE reduces.

(i)  $V_{IF}$  impedance  $R_{in}$  decreased ( $R_{in} = R_1 // R_2 // hFE R_3$ )  $\rightarrow$  signal coupling lower than expected, but is compensated by the margin of the gain.

(ii) base current  $I_B$  req. increases ( $\downarrow hFE$ ,  $I_C$  fixed)  $\rightarrow$  decrease  $R_1, R_2$  values to the revised  $R_3$  hFE value.

## $R_3$ as negative feedback.


- The resistor  $R_3$  provides negative feedback to improve the stability of the circuit (osc., temp. effects and the Early effect (coupling between  $V_{CE}$  and  $V_{BE}$ , i.e.  $\Delta V_{CE} \rightarrow \Delta V_{BE}$ ))

(e.g.  $\downarrow V_B \rightarrow \downarrow I_C \rightarrow \downarrow I_C R_3 \approx V_E \rightarrow V_{CE}$  nonlin., and vice versa  $\rightarrow$  stable bias conditions.)

- Since  $\text{gain} = -\frac{R_2}{R_3}$ , the resistor  $R_3$  reduces the gain. However, we can shunt  $R_3$  w/ a capacitor to effectively remove it from SSM at signal freq.



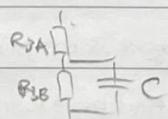At high freq., the above configuration may not be stable, so we can split the resistor as follows.



- \* We choose the capacitor  $C$  to give a low freq. response roll-off

$$f_{3dB} = \frac{1}{2\pi(R_3 // r_e)C}$$

$$f_{3dB} = \frac{1}{2\pi(R_{3B} // (R_{3A} + r_e))C}$$


# For Personal Use Only -bkwk2

## Bipolar Transistor Frequency Response


MILLER EFFECT,

assume it is ideal, i.e.  $i_x = 0$ .

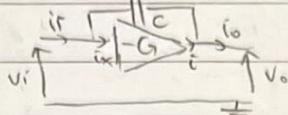- Consider an inverting amplifier ( $W/G \gg 1$ ) w/ some capacitance b/wn its i/p and o/p.



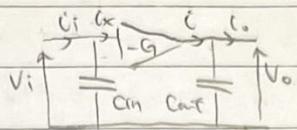We want to find an equivalent capacitor at i/p (to GND) and o/p (to GND)



- summing the currents at the i/p node, (noting  $i_x = 0$  for an ideal amplifier)

$$i_i = \frac{V_i - V_o}{1/j\omega C} = \frac{V_i + G V_i}{1/j\omega C} = \frac{V_i}{j\omega C(1+G)}$$

$$\therefore Z_{in} = \frac{\partial V_i}{\partial i_i} = \frac{1}{j\omega C(1+G)}$$

i.e. the i/p capacitance is equivalent to  $C_{in} = (1+G)C$

- summing the currents at the o/p node,

$$i_o = i + i_{cT} = i + \frac{V_o - V_a}{1/j\omega C} = i - \frac{V_o/G + V_a}{1/j\omega C} = i - \frac{V_o}{j\omega C(1+G)}$$

$$\therefore Z_{out} = \frac{\partial V_o}{\partial i_o} = \frac{1}{j\omega C(1+G)}$$


i.e. the o/p capacitance is equivalent to  $C_{out} = (1+G)C \approx C$ .

- \* The magnification of the capacitance is the Miller effect, and mainly affects the i/p.

$R_T \rightarrow T = R_C \rightarrow$  lower upper 3dB freq. (smaller BW)
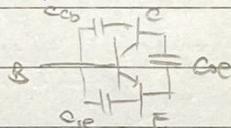
## Bipolar Transistor Terminal Capacitances.

- In practice, transistors have various capacitances b/wn their terminals. For the BJT,



$C_{cb}$  and  $C_{ce}$  are due to a reverse-biased junction and are typically 1-10 pF each.

$C_{be}$  is due to a forward-biased junction and is typically 10-100 pF.

- Actually,  $C_{be}$  depends on the current through the transistor (depletion width in pn junction changes w/ bias), so it is not a single-valued parameter. In fact  $C_{be} \propto I_E \rightarrow C_{be} = k_I E \propto k_I C$ .

- A figure of merit for transistors,  $f_T$ , represents the gain-BW product, and is given by,

$$f_T = \frac{1}{2\pi C_{be} R_E} = \frac{1}{2\pi (k_I E)(0.05 I_C)} = \frac{1}{0.05 \pi k_I} \text{ (const.)}$$

→ Both op. and freq. characteristics of a transistor can be described by just  $I_C$ ,  $f_T$ .



& usually, find  $I_C$  using  $I_C = \frac{V_{CC}/2}{R_E}$  → find  $R_E$  using  $R_E = \frac{V_T}{I_C}$  → find  $C_{be}$  using  $f_T = \frac{1}{2\pi C_{be} R_E}$

# For Personal Use Only -bkwk2

frequency response of standard amplifier circuit.

- consider the standard amplifier circuit (single stage)

circuit

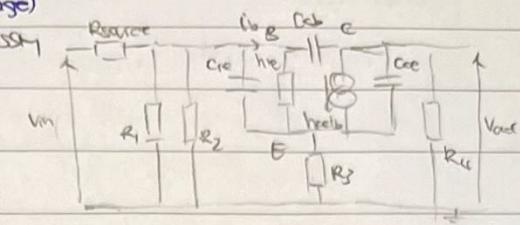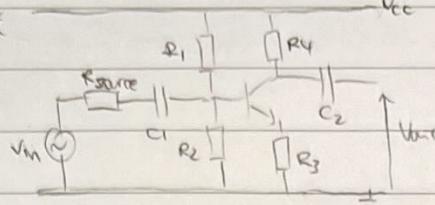

Note that  $C_1$  and  $C_2$  act as short circuits at SSM signal freq.  $\therefore C_{cb}$  and  $C_{ce}$  given in datasheet

$$\text{and } h_{ie} \text{ and } C_{ie} \text{ need to be calculated } (\quad I_c = \frac{V_{ce}}{R_{re}} \rightarrow r_e = \frac{V_e}{I_c} \rightarrow h_{ie} = h_{fe} r_e / C_{ie} = \frac{1}{2\pi f_r C_{ie}})$$

- We can refer impedances connected b/wn B-C/B-E/C-E to B-GND/C-GND using  $\frac{V_o}{V_i}, \frac{V_e}{V_i}, \frac{V_e}{V_o}$ .


$$\hookrightarrow \frac{V_e}{V_i} = -\frac{R_4}{R_3 + r_e} \rightarrow V_{be} = V_i - V_o = V_i + \frac{R_4}{R_3 + r_e} V_i = (1 + \frac{R_4}{R_3 + r_e}) V_i = (1 + G) V_i \rightarrow Z_{eb} = \frac{Z_{re}}{1+G}$$

$$\hookrightarrow \frac{V_i}{V_o} = -\frac{R_3 + r_e}{R_4} \rightarrow V_{cb} = V_o - V_i = V_o + \frac{R_3 + r_e}{R_4} V_o = (1 + \frac{R_3 + r_e}{R_4}) V_o = (1 + \frac{1}{G}) V_o \rightarrow Z_{cb} = \frac{Z_{re}}{1+\frac{1}{G}}$$

$$\hookrightarrow \frac{V_e}{V_i} = \frac{R_3}{R_3 + r_e} \rightarrow V_{be} = V_i - V_e = V_i - \frac{R_3}{R_3 + r_e} V_i = \frac{r_e}{R_3 + r_e} V_i \rightarrow Z_{be} = \frac{Z_{re}}{r_e/R_3 + r_e}$$

$$\hookrightarrow \frac{V_e}{V_o} = \frac{V_e}{V_i} \frac{V_i}{V_o} = -\frac{R_3}{R_4} \rightarrow V_{ce} = V_o - V_e = V_o + \frac{R_3}{R_4} V_o = (1 + \frac{R_3}{R_4}) V_o \rightarrow Z_{ce} = \frac{Z_{re}}{1 + R_3/R_4}$$

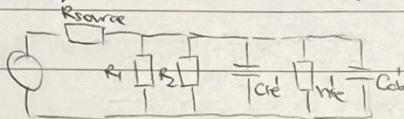- At the i/p, the equivalent SSM circuit becomes.




$$C_{ie}' = \frac{r_e}{R_3 + r_e} C_{ie}, \quad h_{re} = \frac{r_e}{r_e + R_3 + r_e}, \quad C_{cb}' = (1+G) C_{cb}$$

$$R' = R_{source} // R_1 // R_2 // h_{re}, \quad C' = C_{ie}' + C_{cb}'$$

The upper freq. response roll-off is then given by  $f_{dB} = \frac{1}{2\pi R' C'}$

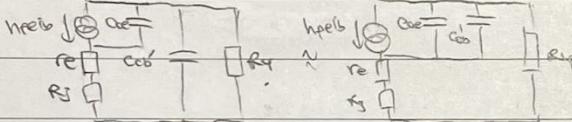- At the Q/P, the equivalent SSM circuit can be approx. as (since  $R_4 \gg R_3 + r_e$ )



$$C_{cb}' = (1+G) C_{cb}$$

$$R' = R_3 + r_e + R_4, \quad C' = C_{ie}' + C_{cb}'$$

The upper freq. response roll-off is then given by  $f_{dB} = \frac{1}{2\pi R' C'}$

- The overall upper freq. response is limited by the lower upper sub freq., which is typically the input.

Increasing the upper sub frequency.

- we can increase the upper sub frequency (and thus increase BW) by circumventing the Miller effect.

- To do so, we req. a pair of resistors.

(i)  $T_1$  is connected to a high impedance source and has unity gain ( $\uparrow R_s, \downarrow C_s \rightarrow \text{small } \gamma$ )


(ii)  $T_1$  is connected to a small impedance source and has a large o/p voltage swing. ( $\downarrow R_s, \uparrow C_s \rightarrow \text{large } \gamma$ )

- Common circuits using the above technique inc. the (modified) differential amplifier and cascode circuit.
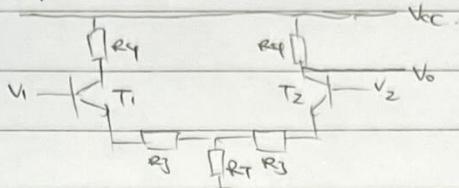
# For Personal Use Only -bkwk2


Differential amplifier.

- The circuit for the differential amplifier is as follows:



$$\text{Note differential gain} = \frac{R_4}{2R_3}, \text{ common-mode gain} = \frac{R_4}{R_3 + 2R_T}, \text{ CMRR} = \frac{2R_T + R_3}{2R_3} \approx \frac{R_T}{R_3} \text{ for } R_T \gg R_3.$$

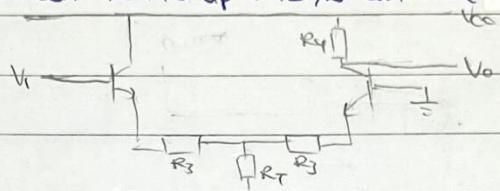
- To circumvent the Miller effect, we ground T2 and take o/p from its collector, while we take the base of T1 as the i/p. Since we don't need the o/p of T1, we can shunt its collector.



\*  $V_1$  causes current swing at T1 emitter  $\rightarrow$  modulates through to T2  $\rightarrow$  voltage swing at T2 collector (o/p).

Cascade circuit.

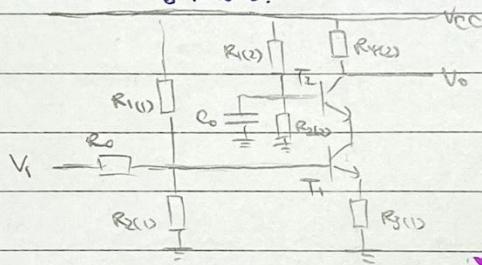- The circuit for the cascade circuit is as follows:




The Miller effect is circumvented since T2 is connected to a fixed voltage w/ low impedance, w/ the o/p taken from T2's collector. The i/p is taken from the base of T1, which does not have any o/p swing at its collector (Vcc is fixed,  $V_{c(1)} \approx V_{c(2)} = 0.7$ ).

\*  $V_1$  causes current swing at T1 collector  $\rightarrow$  modulates through to T2  $\rightarrow$  voltage swing at T2 collector (o/p).


\*  $C_0$  shorts the base of T2 to GND at 50M signal freq. and is chosen using low freq response roll-off.

$$f_{roll-off} = \frac{1}{2\pi(R_{1(2)}/R_{2(2)})C_0}$$

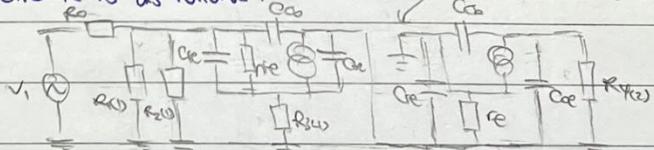
- The OSM for the cascade circuit is as follows:



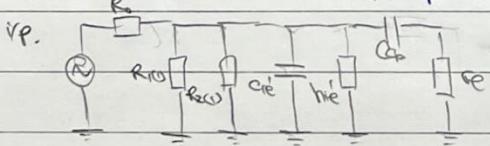The equivalent circuit of the i/p and o/p are shown by


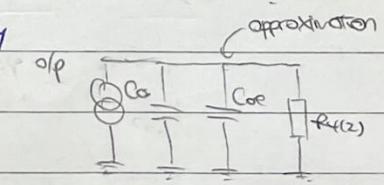
$$R' = (R_0 // R_{1(1)} // R_{2(1)} // h_{ie} + r_e), C' = C_{le} + C_{ce}$$



$$R' = R_{1(2)}, C' = C_{cb} + C_{ce}$$

and the upper 3dB freq. is given by  $f_{3dB} = \frac{1}{2\pi R' C'}$


# For Personal Use Only -bkwk2

## current sources, oscillators and filters

### Current sources
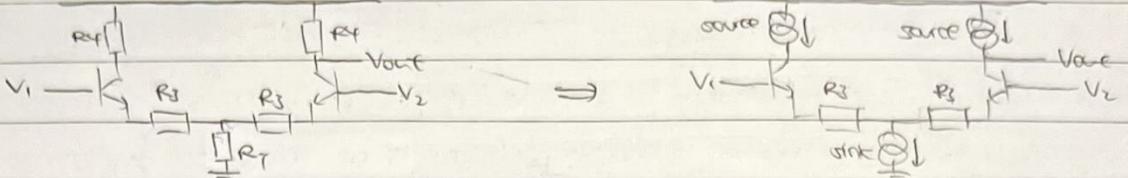
#### Circuit applications for current sources


- In a no. of applications, the use of a current source instead of a simple resistor can improve circuit performance - consider the differential amplifier.



- The CMRR is given by  $CMRR = \frac{R_f}{R_s}$ . If  $R_f$  is replaced by a current source ( $R_f \rightarrow \infty$ ), then  $CMRR \rightarrow \infty$  (w/ DC bias still applied)
- The differential gain is given by  $AG = -\frac{B_2}{2R_s}$ . If  $R_s$  is replaced by a current source ( $R_s \rightarrow \infty$ ) then we get a very high gain.
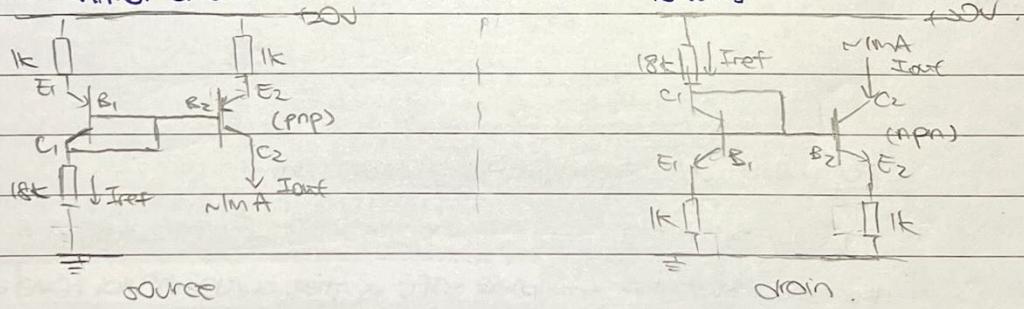
### Current mirror circuits

- A simple current source can be made using a simple FET circuit. However, for more accurate current sources, a current mirror can be used.  $G_{THS} = \frac{V_o}{I} = \frac{1}{R_s}$
- In a current mirror, a reference current is drawn through one of a matched pair of transistors to create a  $V_{BE}$  corresponding to that current.
- This  $V_{BE}$  is then applied to the other transistor, which aims to supply the same collector current as the first, through its own load.
- The current mirror circuits for source/sink are as follows:



$B_1, B_2$  connected;  $E_1, E_2$  same potential (by symmetry)  $\rightarrow V_{BE1} = V_{BE2} \rightarrow I_{C1} = I_{C2}$ .

Assume large  $h_{FE} \rightarrow I_{B1}, I_{B2}$  negligible  $\rightarrow I_{ref} = I_{C1} + I_{B1} + I_{B2} = I_{C1}$

$$I_{out} = I_{C2} = I_{C1} = I_{ref}, \text{ where } I_{ref} = \frac{V_{oc} - V_{BE}}{1k + h_{FE}} \quad [\text{Assume } V_{BE} = 0.7V]$$


- To design a current source, we consider the current sink counterpart, then invert.
- In DSM analysis of the current mirror,  $C_b = 0$  (useful for finding op impedance  $Z_{out}$ , which is simply the impedance b/wn op terminal and GND).

# For Personal Use Only -bkwk2


## Oscillators
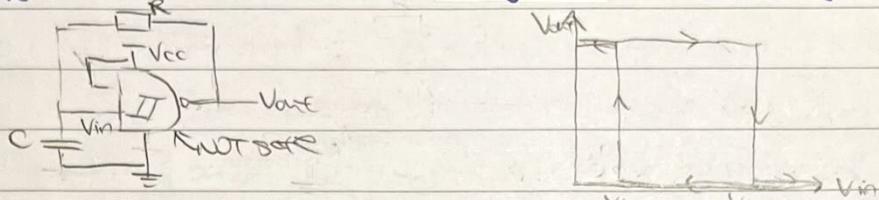
### Relaxation oscillator

- The relaxation oscillator works by charging up a capacitor through a resistor and subsequently discharging it when a threshold is reached.
- For the circuit to work, the threshold detector must have hysteresis (level to turn it on must be higher than the level to turn it off). We can use the Schmidt trigger gate.
- The circuit for the relaxation oscillator and gate transfer characteristics are as follows:



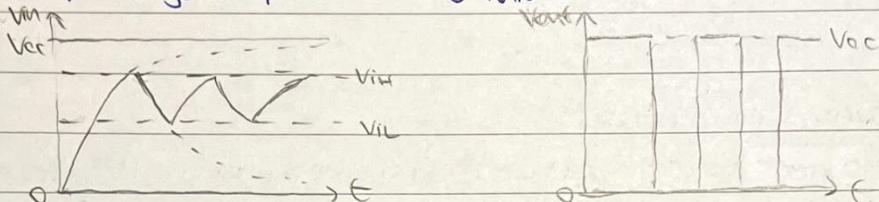- The i/p and o/p voltage vary over time as follows:




i.e. we get a square wave o/p. — this could be integrated to get a triangular wave or filtered to give a sinusoidal o/p (though not very high precision).
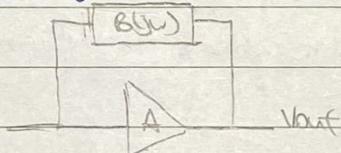
### Positive feedback oscillator

assume const. and does not change the phase

- The positive feedback oscillator involves an amplifier A and passive network B(jω).



- The circuit will sustain stable oscillations when

$$\hookrightarrow (i) |A|B(j\omega) = 1$$


$$\hookrightarrow (ii) \angle A|B(j\omega) = 2k\pi, k \in \mathbb{Z}$$

- For good stability, the phase bode plot of B(jω) should be a sharp function (and |B(jω)|)
- The attenuation of the filter at operating freq. should not be too large as we would need large A.
- To start up the oscillations reliably and maintain them when driving a load, the loop gain |A(jω)| should be  $> 1$  when the oscillation amplitude is low (and vice versa).
- We can implement amplitude/gain control using a variable gain attenuator — oscillation amplitude monitored and used to control the gain of the feedback loop.  
(To avoid distortion of the o/p sine wave, the amplitude control loop should be much slower than the oscillation frequency, i.e. use LPF smoothing filter w/ long time const. T)

# For Personal Use Only -bkwk2
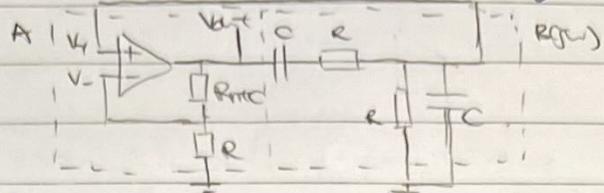
## Wien Bridge oscillator

- A common positive feedback oscillator is the Wien bridge oscillator.



$$\text{where } A = 1 + \frac{R_{FB}}{R} \text{ and } B(j\omega) = \frac{1}{j\omega C + \frac{1}{R_{FB}C}}$$

- To satisfy oscillation condition (i), we req.  $LB(j\omega) = 0$ , which occurs when

$$j\omega CR + \frac{1}{j\omega C} = 0 \rightarrow \omega = \frac{1}{RC}$$


At this frequency, to satisfy oscillation condition (ii), we req.  $A \cdot \frac{1}{3} = 1$ , which occurs when

$$1 + \frac{R_{FB}}{R} = 3 \rightarrow A_{FB} = 2R.$$

- For amplitude control, a -ve temp. coeff. thermistor is used ( $\uparrow$  oscillation amplitude)

$\rightarrow \uparrow$  power dissipated  $\rightarrow \uparrow T \rightarrow \downarrow R_{FB} \rightarrow \downarrow A$ , and vice versa).

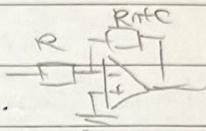- In general, to use  $R_{FB}$  to provide -ve FB, place it at. gain  $\propto R_{FB}$ .



(Alternatively, a variable gain attenuator would work as well.)


## Digital clock oscillator

- To build a high stability oscillator for fixed freq. (eg. time references), a quartz crystal is usually used ( $R, C$  have non-zero temp. coeff.  $\rightarrow$  unstable w/ large temp. variations).

The device is a specifically shaped piece of quartz which has a mechanical resonance at a particular freq. Since quartz is piezoelectric, we have an electrically resonant circuit.

- The Q-factor of a quartz crystal is typically  $\sim 10^3$  and the temp. stability is good  $\approx 10^{-9}/^\circ\text{C}$ .

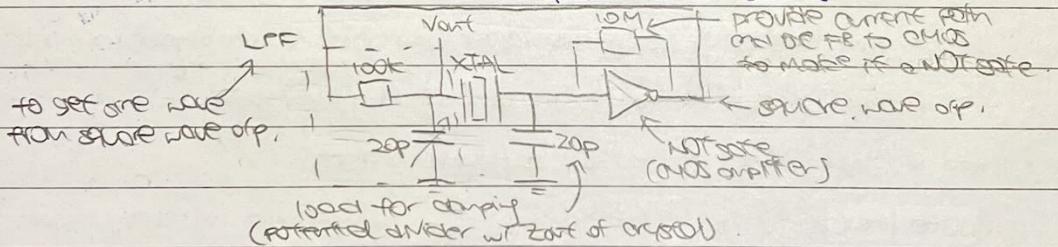- The circuit for the digital clock oscillator is as follows:




## RF oscillator

- To tune a radio oscillator (vary RC resonant freq.) electronically, we can use varactors

(based on the variable capacitance of a reverse-biased pn junction)

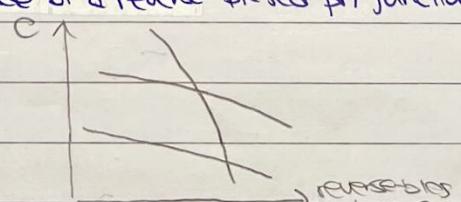
charge bias  $\rightarrow$  charge width of depletion region  $\rightarrow$  vary C [Early effect].



$\rightarrow$  we get a voltage-controlled oscillator (VCO)

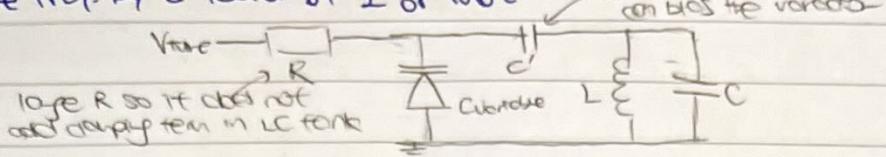
# For Personal Use Only -bkwk2

- By including the capacitance of a varactor in a LC tank circuit, we can tune the freq. by a factor of 2 or more.



so we have  $C_{eff} = C + C_{variable}$  (Note  $C' \gg C_{variable} \rightarrow$  negligible)

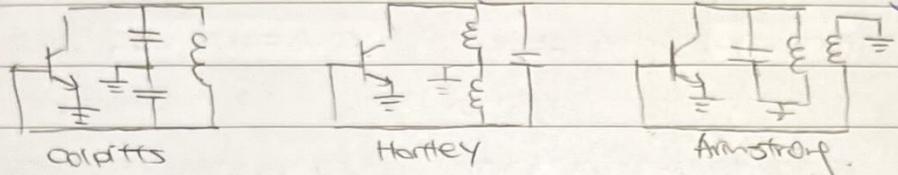
- Popular configurations for RF circuits include Colpitts, Hartley and Armstrong.



All of these can be tuned electronically by coupling a varactor across the LC resonant circuit.
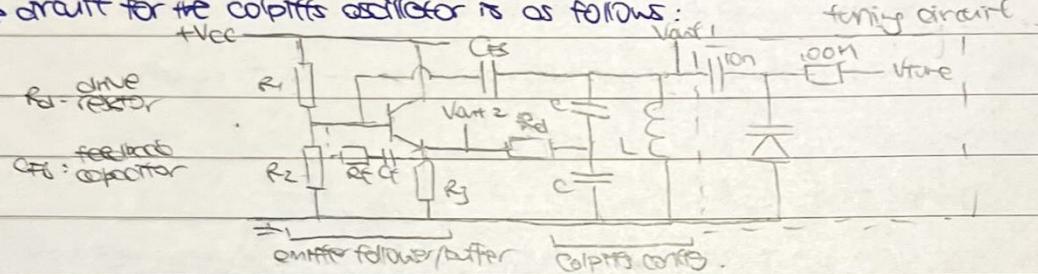
## Colpitts oscillator


- The circuit for the Colpitts oscillator is as follows:



The use of two series capacitors across the inductor, to create the LC tank w/ separate drive and FB pts from/to the transistor is the hallmark of the Colpitts design.

(We have an emitter follower ( $\text{gm} \sim 1$ ) driving the LC network ( $\text{gm} \sim 2$ ) for the FB loop)

- We can take the op from two convenient pts:
  - ↳  $V_{out1}$ : min. distortion, but only for high impedance loads (otherwise use a buffer)
  - ↳  $V_{out2}$ : higher op power and better load isolation, but higher harmonic distortion (minimized using  $R_E$ )
- If we add a base-emitter load impedance ( $R_E + \text{DC blocking } C_E$ ), we set the emitter swing to  $\sqrt[3]{2}$  supply voltage  $\rightarrow$  less harmonic distortion.
- $R_1, R_2$  appear across LC tank in SSM  $\rightarrow$  dampen the response, lower Q.
- $C_{FB}$  act as a DC block to prevent L from shorting the base to GND.
- At resonance, the LC network acts as a 2:1 transformer, so a load  $R_L$  across the inductor ( $V_{out1}$ ) referred to the emitter will be  $\frac{Z_L}{2} = \frac{Z_L}{4}$ .

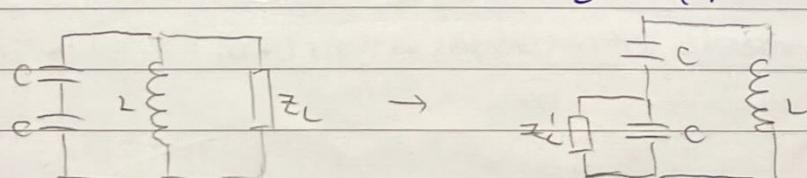

# For Personal Use Only -bkwk2

Designing a Colpitts oscillator.

## ① Power level

- check that  $V_{pp} < 60\%$  of  $V_{cc}$ .

## ② Select transistor and set DC bias resistors.

- choose a low power NPN transistor w/  $f_t \gg$  req. freq.  $\checkmark \sim 50 \text{ MHz}$ .

- set base bias  $V_B$  to give  $V_E \approx \frac{1}{2}V_{cc}$  for max. voltage swing,  $V_E = V_B - 0.7$

- If we use  $V_{out2}$ , refer load impedance to emitter  $V_{out2}$ ,  $Z'_L = \frac{Z_L}{2} = \frac{Z_L}{4}$ .

- choose  $R_3 \approx 1.5 - 2 \times Z'_L$  (use  $Z_L$  referred at emitter  $V_{out2}$ )  $(\sim 10^2)$

- choose  $R_1$  and  $R_2 \approx h_{fe} \times (R_3 // Z'_L)$  and use  $V_B = V_{cc} \frac{R_2}{R_1 + R_2}$  (use  $Z_L$  referred at emitter  $V_{out2}$ )  $\checkmark$  Impedance looking at the base.

## ③ Select L & C and varactor

- consider total C tuning ratio,  $\frac{C_{out}}{C_{min}} = \left( \frac{f_{max}}{f_{min}} \right)^2$  [since  $f \propto \sqrt{LC}$ ]

- $C_{FS}$  is large — just to block DC, low impedance at signal freq. range, (e.g.  $\sim 10 \text{ nF}$ )

- select a varactor (e.g. IN5476A,  $C_{var,max} = 200 \text{ pF}$ ,  $C_{var,min} = 10 \text{ pF}$ )

choose  $C \approx 1.5 - 2 \times C_{var,max}$ , then check  $\frac{C_{out}}{C_{min}} = \frac{C/2 + C_{var,max}}{C/2 + C_{var,min}}$  is larger than requirement.

- choose  $L = \frac{1}{(2\pi f_{min})^2 C_{mid}}$ , where  $f_{mid} = \frac{f_{max} + f_{min}}{2}$ ,  $C_{mid} = \frac{C_{var,max} + C_{var,min}}{2} + \frac{C}{2}$

## ④ LC network drive resistor.

must be less than  $1/4$

- select  $R_d \leq \frac{1}{4} \times (\text{all resistors} // L) = \frac{1}{4} (R_1 // R_2 // h_{fe} R_3 // h_{fe} Z_L // \omega L Q_2)$

\* Note  $R_d$  too small  $\rightarrow$  distortion;  $R_d$  too big  $\rightarrow$  loop gain  $< 1$

$\checkmark \sim 50$

e.g. Design an oscillator circuit for a radio tuner, tuning range 595-755 kHz.

o/p power 5dBm into  $300 \Omega$ , supply 5V. [Note dBm is dB rel to 1mW]

$$\textcircled{1} . \quad 5 \text{ dBm} = 3.2 \text{ mW} = \frac{V_{rms}^2}{Z_L}, \quad Z_L = 300 \Omega \rightarrow V_{rms} = 0.95 \text{ V} \rightarrow V_{pp} = 2\sqrt{2} V_{rms} = 2.68 \text{ V}.$$

$$V_{pp} = 2.68 \text{ V} < 3 \text{ V} = 0.6 V_{cc} \rightarrow \text{OK!}$$

$$\textcircled{2} . \quad \text{set } V_E = \frac{1}{2} V_{cc} = 2.5 \text{ V} \rightarrow V_B = 2.5 + 0.7 = 3.2 \text{ V}.$$

$$\text{choose } R_3 = 1.75 Z_L = 525 \Omega$$

$$\text{choose } R_1, R_2 \approx h_{fe} (R_3 // Z_L) = 47.7 \text{ k}\Omega, \text{ and } V_B = V_{cc} \frac{R_2}{R_1 + R_2}, \text{ say } R_1 = 45 \text{ k}\Omega, R_2 = 80 \text{ k}\Omega$$

\* Assume the chosen transistor has  $f_t = 250 \text{ MHz}$ ,  $h_{fe} = 250$ , for BC182L

$$\textcircled{3} . \quad \frac{C_{out}}{C_{min}} = \left( \frac{f_{max}}{f_{min}} \right)^2 = 1.78$$

$$\text{choose } C_{FB} = 10 \text{ nF}, \text{ varactor w/ } C_{var,max} = 200 \text{ pF}, C_{var,min} = 10 \text{ pF}.$$

$$\text{choose } C = 1.75 \times 300 = 525 \text{ pF.} \rightarrow \frac{C_{out}}{C_{min}} = \frac{C/2 + C_{var,max}}{C/2 + C_{var,min}} = 2.06 > 1.78 \rightarrow \text{OK!}$$

$$f_{mid} = \frac{f_{max} + f_{min}}{2} = 675 \text{ kHz}, \quad C_{mid} = \frac{C_{var,max} + C_{var,min}}{2} + \frac{C}{2} = 417.5 \text{ pF.}$$

$$\text{so } L = \frac{1}{(2\pi f_{mid})^2 C_{mid}} = 133 \text{ nH.}$$

$$\textcircled{4} . \quad R_d \leq \frac{1}{4} (R_1 // R_2 // h_{fe} R_3 // h_{fe} Z_L // \omega L Q_2) = 2.2 \text{ k}\Omega \rightarrow \text{choose } R_d = 2 \text{ k}\Omega.$$


\* choose coupling capacitor from varactor to be  $C = 10 \text{ nF}$ , varactor resistor to be  $10 \text{ M}\Omega$

# For Personal Use Only -bkwk2
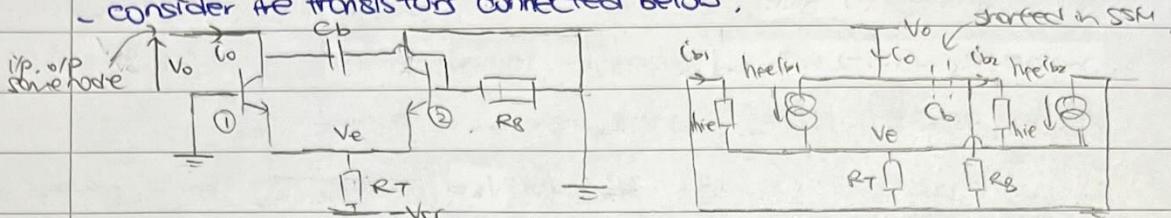
## Negative impedance oscillator

- The negative impedance oscillator is commonly used at high freq. (up to GHz)
- A pair of (FET) transistors can be configured to give an apparent  $-V_o$  resistance
- If connected across LC tank circuit, the  $-ve$  resistance compensates for the circuit's resistive losses → resonant LC oscillations do not die away (from damping).

- consider the transistors connected below,




$$i_{b1} = -\frac{V_e}{h_{fe}} ; i_{b2} = \frac{V_o - V_e}{h_{fe}} ; i_o = h_{fe}i_{b1} + i_{b2} + \frac{V_o}{R_B} ; V_e = (h_{fe})(i_{b1} + i_{b2})RT$$

$$\therefore V_e = \frac{h_{fe}}{h_{fe} + 1} RT (-V_e + V_o - V_e) \rightarrow V_e \left( \frac{2h_{fe}}{h_{fe} + 1} RT \right) = \frac{h_{fe}}{h_{fe} + 1} RT V_o \rightarrow V_e = \frac{V_o}{2}$$

$$\therefore i_o = h_{fe} \left( -\frac{V_e}{h_{fe}} \right) + \frac{V_o - V_e}{h_{fe}} + \frac{V_o}{R_B} = -\frac{h_{fe}}{2h_{fe}} V_o + \frac{V_o}{2h_{fe}} + \frac{V_o}{R_B} = \left[ \frac{1}{2h_{fe}} (h_{fe} + 1) + \frac{1}{R_B} \right] V_o$$

$$\Rightarrow Z_o = \frac{V_o}{i_o} = \left[ \frac{1}{R_B} - \frac{h_{fe}}{2h_{fe}} \right]^{-1} = \left[ \frac{1}{R_B} + \frac{1}{2h_{fe}} \right]^{-1}, \text{ i.e. } Z_o = R_B // -2h_{fe}.$$

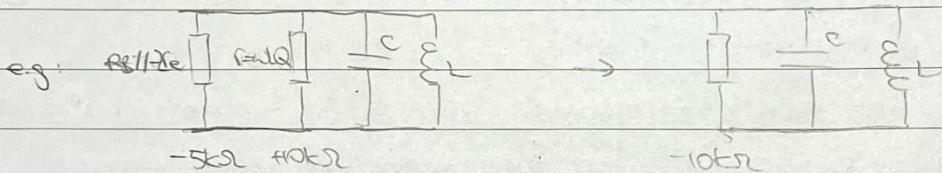- Therefore, we can make a negative impedance based oscillator circuit by adding a suitable tuned LC circuit (where resistive parasitic component is cancelled out)




- The LC combination w/  $-ve$  parasitic impedance is inherently unstable → lead to oscillations.

- The amplitude of oscillation grows exponentially, until the voltage swing across the resistors prevents them from reducing the effective  $-ve$  impedance → steady oscillations.

(For transistors, Voltage swing → ↓ gain, so steady state).

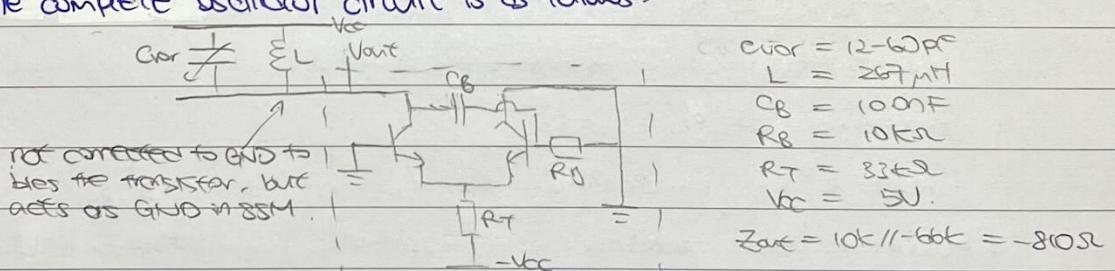- The complete oscillator circuit is as follows:



-ve impedance network



\* Intuition for -ve impedance:  $\uparrow V_o \rightarrow \uparrow V_{B2} \rightarrow \uparrow V_{E2} \rightarrow \downarrow V_{BE1} \rightarrow \downarrow I_{C1} \rightarrow \downarrow i_o$

# For Personal Use Only -bkwk2

## Filters

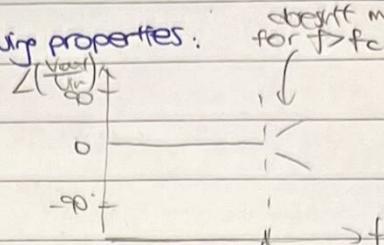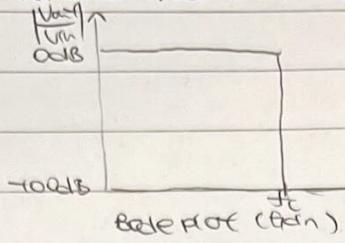
### The ideal filter

- An ideal filter has the following properties:



doesn't matter  
for  $f > f_c$

step w/o overshoot.

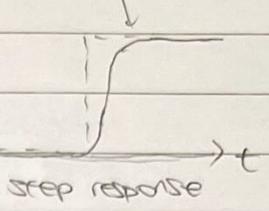


This would be ideal for extracting almost any signal from noise, whilst also retaining the original waveform shape. (Real filters have trade-off b/w freq/time domain performance)


### Passive RC filters

- The simplest filter arrangement comprises the passive RC filter.

LOW PASS

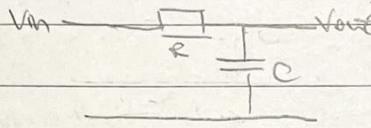

HIGH PASS

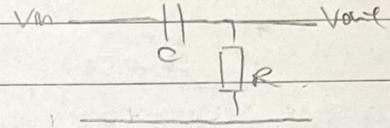


$$\frac{V_{out}}{V_{in}} = \frac{1}{1 + j\omega RC}$$

$$\frac{V_{out}}{V_{in}} = \frac{1}{1 + j\omega RC}$$

- These are fine for non-demanding applications, where the desired signal freq. is very diff. to that of the background noise / interference (rare in practice)
- For two freq. fairly close to each other, say 10% diff.,  $f_2 = 1.1f_1$ , a RC filter set w/ a 3-dB roll-off at  $f_1$  only attenuates the  $f_2$  signal by 5% more (we want  $>100\times$  attenuation)
- (Even cascading 10 stages using buffers only attenuates the  $f_2$  signal by 40% more)
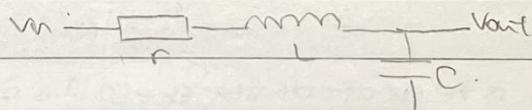
### Resonant LC filters

- The circuit of the resonant LC circuit is as follows:



$$\frac{V_{out}}{V_{in}} = \frac{V_{out}}{V_{out} + V_{in}} = \frac{1}{1 - \omega^2 LC + j\omega CR}, \quad Q = \frac{1}{\omega_0 CR} = \frac{\omega_0 L}{R}, \text{ where } \omega_0 = \frac{1}{\sqrt{LC}}$$

$$\rightarrow \frac{V_{out}}{V_{in}} = \frac{1}{1 - (\omega/\omega_0)^2 + j/Q(\omega/\omega_0)} \quad \therefore \text{ If } \omega = \omega_0, \left| \frac{V_{out}}{V_{in}} \right| = Q.$$

(Note if  $Q=100$ , for  $\omega=1.1\omega_0$ ,  $\left| \frac{V_{out}}{V_{in}} \right| = 4.76 \approx 0.05 Q \rightarrow$  good selectivity b/w freq.)

- However, there are a few practical problems associated w/ inductors:

↳ Large values (for small  $\omega_0$ ) are physically large and rel. expensive.


↳ They are often lossy, have stray capacitance and are nonlinear

↳ They act as weakly-coupled transformers → pick up interference from stray B fields → noise
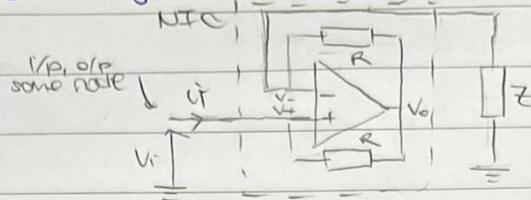
# For Personal Use Only -bkwk2

Negative impedance circuit.

- The circuit for the negative impedance converter (NIC) is as follows:



For ideal opamp,  $V_+ = V_- \rightarrow V_i = V_-$


$$\sum i_+ : i_+ - \frac{V_i - V_o}{R} = 0 \quad ; \quad \sum i_- : \frac{V_i - V_o}{R} + \frac{V_o}{Z} = 0,$$

$$\text{Eliminating } V_o, \quad \frac{V_i}{R} - i_+ = V_i \left( \frac{1}{Z} + \frac{1}{R} \right) \rightarrow Z_{in} = \frac{V_i}{i_+} = -Z$$

$\rightarrow$  Impedance looking into the circuit is the negative of the impedance  $Z$  of the circuit.

\* If  $Z$  is a capacitor  $\frac{1}{j\omega C}$  then  $Z_{in} = \frac{j}{\omega C}$  (not quite an inductor as  $Z \propto \frac{1}{j\omega}$ , not  $Z \propto \omega$ ).

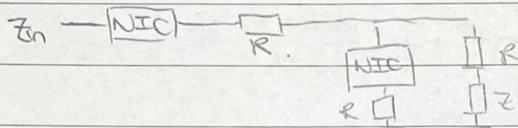- If we want a true inductor, we can connect a pair of NICs as follows (gyrator):



$$Z_{in} = - \left( R + \frac{R(R+Z)}{R+R+Z} \right) = - \left( R - \frac{R^2}{Z} - R \right) = \frac{R^2}{Z}$$

If  $Z$  is a capacitor  $\frac{1}{j\omega C}$ , then  $Z_{in} = j\omega CR^2$ , i.e. an inductor w/  $L = CR^2$ .

- To make an inductor w/ both ends floating, string a pair of gyrator circuits back-to-back, sharing the same series  $Z$  at the centre.

asked)

\* The synthetic inductor only looks like an inductor while the opamps are behaving correctly (i.e. within the freq. range / voltage swing of the opamp).

(we rep. gain control as voltage swing  
→ gain const. → clipping occurs.)

Bessel, Butterworth and Chebyshev filters.

$$s = j(f/f_c)$$


- Three common types of n-pole only filters include:

- ↳ 1) Bessel  $\left| \frac{V_o}{V_i} \right| = 10^{-\frac{2}{n} \left( \frac{f}{f_c} \right)^2}$  for  $\frac{f}{f_c} < 2$  e.g.  $H(s) = \frac{H}{0.0075s^4 + 0.752s^3 + 0.483s^2 + s + 1}$
- ↳ 2) Butterworth  $\left| \frac{V_o}{V_i} \right| = \left( 1 + \left( \frac{f}{f_c} \right)^n \right)^{-1/2}$  e.g.  $H(s) = \frac{H}{s^4 + 2.613s^3 + 3.414s^2 + 2.613s + 1}$
- ↳ 3) Chebyshev  $\left| \frac{V_o}{V_i} \right| = \left( 1 + \epsilon^2 C_n^2 \left( \frac{f}{f_c} \right)^n \right)^{-1/2}$  e.g.  $H(s) = \frac{H}{3625^4 + 3.455^3 + 527s^2 + 269s + 1}$

↑ Coeff of  $s^n$ ,  
faster the roll-off

where  $\epsilon \in [0, 1]$  is the shape factor;  $C_n(f_c)$  is the Chebyshev polynomial of order  $n$  for  $(f/f_c)$

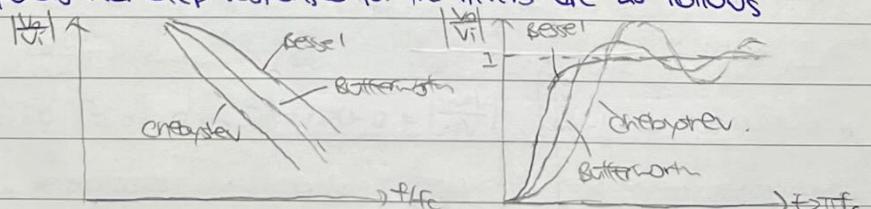- The freq. response and step responses for the filters are as follows



- The optimum choice of filter for a particular application depends on the rel. importance of freq. and time performance.

↳ Bessel: passing transients undistorted

↳ delay all freq. by the same amount → no distortion


↳ Butterworth: fair compromise b/w the two - general all-rounder.

↳ Chebyshev: sharp freq. cut-off
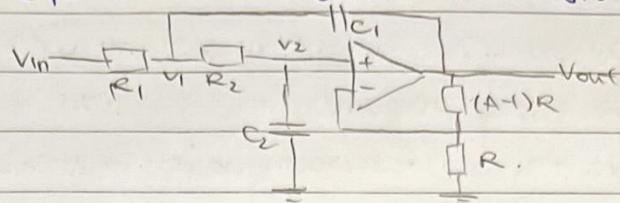
# For Personal Use Only -bkwk2

Voltage-controlled voltage source (VCVS) filter.

- consider the low-pass 2-pole VCVS filter (butterfly topology)



For convenience, choose  $C_1 = C_2 = C$ ,  $R_1 = R_2 = R$ .

$$V_o = AV_2 ; \quad V_2 = V_i \frac{1}{1+j\omega CR} ; \quad \frac{V_i - V_2}{R} = \frac{V_i - V_2}{j\omega C} + \frac{V_o - V_2}{R} \rightarrow V_i = V_o(2+j\omega CR) - V_o j\omega CR - V_2$$

$$\therefore V_i = \frac{1+j\omega CR}{A} V_o (2+j\omega CR) - V_o j\omega CR - \frac{V_o}{A} = \frac{V_o}{A} [1 - (\omega CR)^2 + j\omega CR(3-A)]$$

$$\rightarrow \left| \frac{V_i}{V_o} \right| = A \left[ (1 - (\omega CR)^2)^2 + (\omega CR)^2 (3-A)^2 \right]^{-1/2} = A \left[ 1 + (\omega CR)^2 [(3-A)^2 - 2] + (\omega CR)^4 \right]^{-1/2}$$

$$= A \left[ 1 + \left(\frac{\omega}{\omega_n}\right)^2 B + \left(\frac{\omega}{\omega_n}\right)^4 \right]^{-1/2} \quad \text{where } B = (3-A)^2 - 2, \quad \omega_n = \frac{1}{CR}$$

(Note for  $B=0$ , we have the Butterworth filter).

- Therefore, depending on the choice of  $A$  and  $CR = \frac{1}{\omega_n}$ , a range of filter characteristics can be provided w/ this circuit, w/ higher orders realised by cascading several stages.
- (no. of stages =  $\frac{\text{no. of poles } n}{\text{poles per stage}} = \frac{n}{2}$ ).

- The table of req. cut-off freq. settings to achieve a particular filter characteristic is as follows:

no. of poles $n$	Bessel		Butterworth		Chebyshev	
	$f_n$	$A$	$f_n$	$A$	$f_n$	$A$
2	1.274	1.268	1	1.586	1.231	1.842
4	1.482	1.084	1	1.152	0.597	1.582
	1.606	1.759	1	2.235	1.031	2.660
6	1.607	1.070	1	1.068	0.396	1.557
	1.622	1.364	1	1.586	0.708	2.548
	1.908	2.023	1	2.583	1.011	2.946

where the  $f_{nB}$  for each stage is given by  $f_{nB} = \frac{1}{2\pi f_n C R}$   $\rightarrow f_{nB} = \frac{1}{2\pi (V_o f_n) C R}$

- High pass filters are realised by swapping over  $R_s$  and  $C_s$  & use  $f_n' = \left(\frac{f_n}{f_n}\right)$  to find  $CR$ .
- Band pass filters are made by cascading overlapping low pass and high pass stages.

VCVS filter design


benefits and drawbacks  
of each filter type.

- Determine the type of filter (based on problem req.) and no. of poles  $n$  (based on ref. SNR/attenuation)  $\rightarrow$  Find  $f_n$  and  $A$
- Determine the req. cut-off freq.  $f_c$  from the problem (if given the rise time  $t_{rise}$ , use  $t_{rise} \geq 2.2\tau$ ,  $f_c = \frac{1}{2\pi\tau} \rightarrow f_c = \frac{2.2}{2\pi t_{rise}}$ )  $\rightarrow$  Find  $CR$  (usually set  $R=10k\Omega$ )
- Design a BPF by combining a LPF and HPF.

# For Personal Use Only -bkwk2

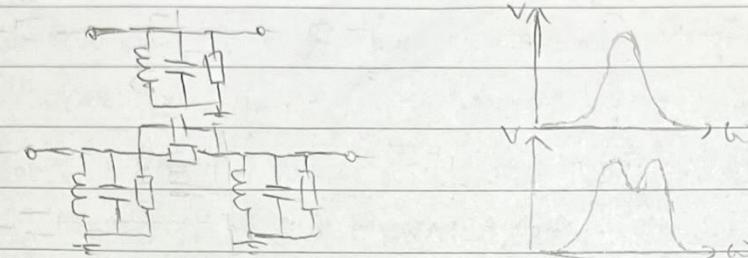
## Ceramic and surface acoustic wave (SAW) filters

- Ceramic and SAW filters rely on the piezoelectric effect. Exotic materials like  $\text{LiNbO}_3$  and  $\text{LiTaO}_3$  are used in addition to quartz to achieve high Q factors ( $>1000$ )
- ceramic filters are coupled resonator filters — a no. of resonant discs w/ diff. resonant freq. are mechanically coupled together w/ top and bottom electrodes deposited onto each end of the stack.
- the operation of a ceramic filter can be modelled as cascading LC circuits.



w/ more stages we can get a flatter top, steeper band edges and wider BW.

- For SAW filters, instead of bulk acoustic waves passing through the dielectric, surface waves are propagated in the top few microns along the crystal surface.
- The waves are created and detected by a series of interdigitated electrode patterning — the E-field b/w the electrodes stresses the material to produce a SAW.
- If the pitch (spacing) of the electrodes is correct, then the acoustic signal is converted back into an electrical signal at the o/p (only certain freq. pass  $\rightarrow$  filter)

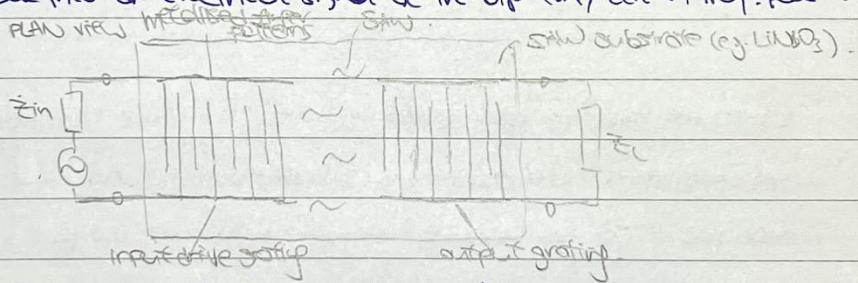

- To detect/create a wave w/ wavelength  $\lambda$ , the electrodes should have a pitch of  $\lambda/2$  spacing and  $\lambda/4$  width [ $\lambda$  found from  $v=f\lambda$ ]
- BW control using variation in grating pitch (increase the pitch gradually, re. "chirp")

# Mixers and phase-locked loops For Personal Use Only -bkwk2

## Mixers

Mixers as analog multipliers

- The mixer is an analog voltage multiplier, consider the trigonometric relation

$$\sin A \sin B = \frac{1}{2} \cos(A-B) - \frac{1}{2} \cos(A+B)$$

- For i/p s w/ diff. freq, the o/p contains the sum and diff. terms  $f_1 + f_2$ ,  $f_1 - f_2$

$$A = 2\pi f_1 t, B = 2\pi f_2 t \rightarrow \sin A \sin B = \frac{1}{2} \cos(2\pi(f_2 - f_1)t) - \frac{1}{2} \cos(2\pi(f_1 + f_2)t)$$

- For i/p s have the same freq, the mixer behaves as a phase detector (DC component in the o/p related to the phase shift btwn the i/p s)


$$A = 2\pi f t, B = 2\pi f t + \phi \rightarrow \sin A \sin B = \frac{1}{2} \cos \phi - \frac{1}{2} \cos(2\pi(\phi)t)$$

## Ideal mixer properties

- In principle, any nonlinear component can be used as a mixer (applying a sine wave to a device w/ changing slope on I-V curve distorts it  $\rightarrow$  produces harmonics)
- However, when issues like efficiency, noise isolation btwn terminals, freq. resp., etc. are considered, then the choice of mixer circuit becomes critical for good performance.
- An ideal mixer has the following properties (in RF applications)
  - ↳ Isolation of LO, IF and RF
  - ↳ No harmonic distortion
  - ↳ Low conversion loss (rel. to ratio of o/p to i/p power)
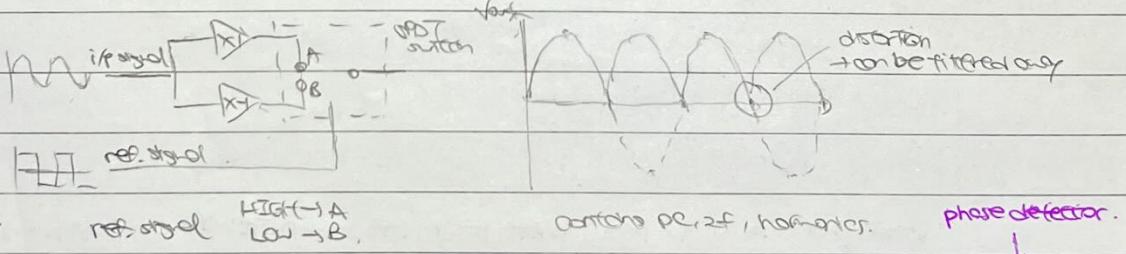
## Inverting/non-inverting amplifier mixer

- An inverting/non-inverting amplifier mixer involves a ref. signal switching the state of the amplifier btwn the two polarities
- If the ref. signal has the same freq. and phase as the i/p signal, then we have active rectification, where the -ve cycles are inverted to be +ve.



\* Verify the phase diff. btwn i/p s from 0° to 90° varies DC component from max to 0.

- This circuit is used up to 10 MHz for phase-sensitive detection, lock-in amplifiers and synchronous detection (ref. signal is a square wave of unity amplitude)

- The XOR gate has the same function where both signals are digital  $\rightarrow$  if o/p of XOR gate is LPFed to remove AC components, we have a square wave phase comparator.


# For Personal Use Only -bkwk2

## Mixer topologies

- Mixers may be classified by their topology
  - ↳ Unbalanced mixer : in addition to producing a product signal, allowing both i/p signals to pass through and appear as components in the o/p.
  - ↳ Single-balanced mixer : one of its i/p's is applied to a balanced circuit  $\rightarrow$  either LO or RF is suppressed at the o/p, but not both
  - ↳ Double-balanced mixer : both i/p's are applied to a balanced circuit  $\rightarrow$  neither i/p signal (only the product signal) appears at the o/p.

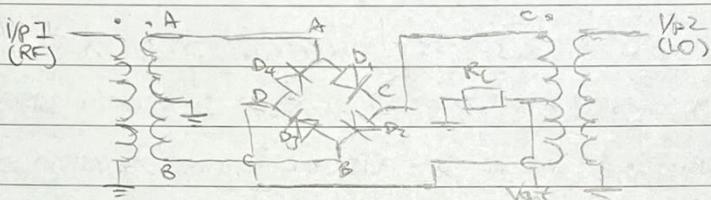
## Double balanced mixer

- The circuit for the double balanced mixer is as follows :



(Note the diodes are connected in a ring NOT like a bridge rectifier)

- When i/p 1 swings into the half cycle :
  - ↳ A swings +ve, & swings -ve (by some amt) due to GND at coil midpt.
  - ↳ D<sub>1</sub>, D<sub>2</sub> conducts  $\rightarrow$  C is GND ; D<sub>3</sub>, D<sub>4</sub> blocks  $\rightarrow$  D is floating at high impedance
  - ↳ If i/p 2 is in phase w/ i/p 1  $\rightarrow$  C swing +ve wrt coil midpt  $\rightarrow$  D swing -ve wrt GND.
- (The opposite occurs when i/p swings into -ve half cycle)
- Effectively, when i/p 1 is +ve, i/p 2 is flipped, and vice versa.

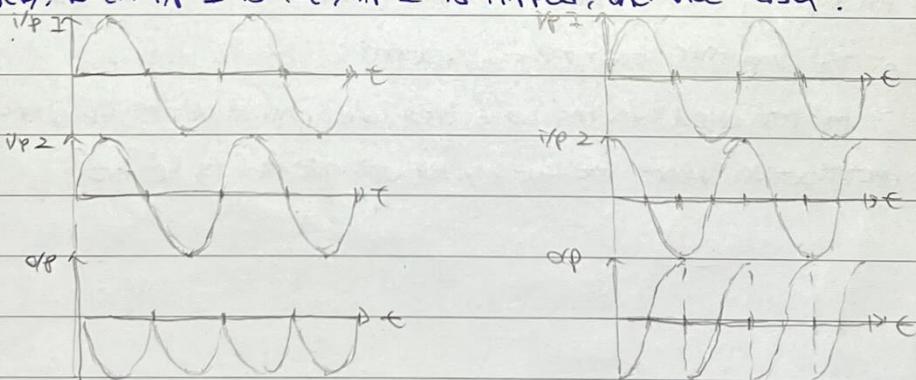

- When there is a 90° phase shift b/w i/p's, then the o/p contains no DC.

For diff. i/p freq, there is a continuously changing phase diff.  $\rightarrow$  DC term becomes beat freq.


(If we have i/p freq. f<sub>1</sub> and f<sub>2</sub>, we get o/p freq. (f<sub>1</sub>-f<sub>2</sub>) and f<sub>1</sub>+f<sub>2</sub>)

- ↳ Double balanced mixers are rel. expensive as they have transformers.

# For Personal Use Only -bkwk2

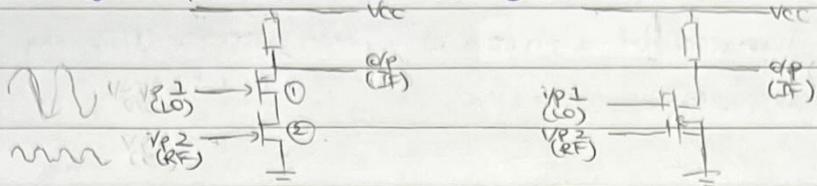**cascade and dual gate MOSFET mixer (single balanced mixer)**


- THE CIRCUITS FOR THE CASCADE AND DUAL GATE MOSFET MIXER ARE AS FOLLOWS:



- THE RF I/P TO GATE OF FET 2 MODULATES ITS DRAIN CURRENT, WHICH PASSES THROUGH FET 1 AS WELL.
- THE LO I/P TO GATE OF FET 1 CHANGES ITS RESISTANCE.
- SINCE  $V = IR$ , THE VOLTAGE O/P IS A PRODUCT OF RF AND LO SIGNALS  $\rightarrow$  MIXER.
- THE DUAL-GATE MOSFET WORKS THE SAME WAY BUT THE TRANSISTORS ARE IN ONE DEVICE W/ TWO GATES.
- ALTHOUGH ISOLATION IS GOOD BTWN RF/LO I/P'S, THERE IS STRONG FEEDBACK OF LO I/P TO RF O/P (IN ADDITION TO THE SUM AND DIFFERENCE TERMS).
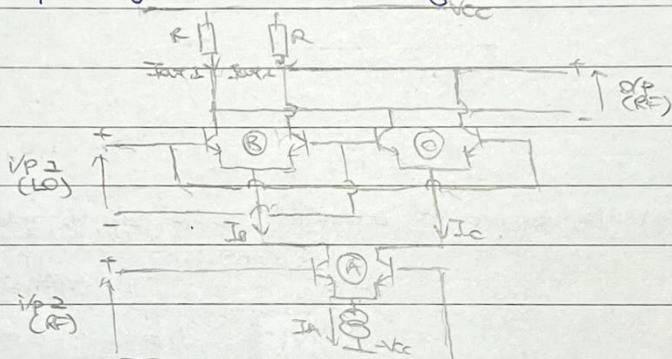
## Gilbert Cell Mixer

- THE GILBERT CELL MIXER INCLUDES A PAIR OF SINGLE BALANCED MIXERS, CONNECTED DIFFERENTIALLY W/ THE O/P'S SUMMED - SYMMETRY OF ARRANGEMENT CANCELS DIRECT THROUGHPUT OF LO, RF SIGNALS.



- THE LOWER DIFF. AMPLIFIER A STEERS THE CURRENT  $I_A$  FROM SIDE TO SIDE BTWN THE UPPER DIFF. AMPLIFIERS B, C..
- THE UPPER DIFF. AMPLIFIERS B, C THEN STEER THEIR RESPECTIVE TAIL CURRENTS  $I_B, I_C$  BTWN THEIR TWO O/P'S, WHICH ARE CROSS-COUPLED  $\rightarrow$  NEITHER LO OR RF I/P DIRECTLY COUPLED TO IF O/P.


- IF THE RF I/P STEERS  $I_A$  IN THE RATIO  $k_1 : 1-k_1$ , AND LO I/P STEERS  $I_B, I_C$  IN THE RATIO  $k_2 : 1-k_2$ ,

$$I_B = k_1 I_A \quad ; \quad I_C = (1-k_1) I_A \quad ; \quad I_{out,1} = k_2 I_B + (1-k_2) I_C \quad ; \quad I_{out,2} = (1-k_2) I_B + k_2 I_C$$

$$V_{out} = (I_{out,2} - I_{out,1}) R = I_A [k_1(1-k_2) + (1-k_1)k_2 - k_1k_2 - (k_1)(1-k_2)] = I_A (2(k_1+k_2) - 4k_1k_2 - 1)$$

$\rightarrow$  IF  $k_1=k_2$  or  $k_1=1-k_2$  (NO LO RF SIGNAL), THEN  $V_{out}=0$ , AS REQ.

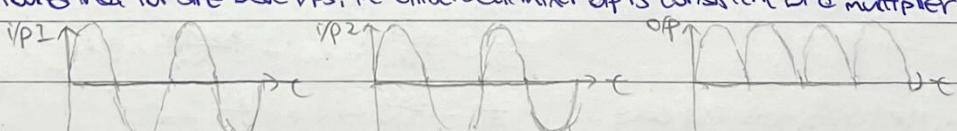- IT IS FOUND THAT FOR sine WAVE I/P'S, THE GILBERT CELL MIXER O/P IS CONSISTENT W/ A MULTIPLIER.



# For Personal Use Only -bkwk2

## Phase locked loops (PLL)

### Phase locked loops (PLL)


- The PLL is a FB loop consisting of a phase detector (PD), loop filter and voltage-controlled oscillator (VCO)



- The PD compares the phase of the i/p w/ the VCO o/p and produces a phase error signal w/ a DC component
- The error signal is filtered and fed to the VCO s.t. the freq. and phase o/p/s of the VCO,  $w_o, \theta_o$  track and lock on to the i/p signal.
- The PLL has "freq. inertia" — the VCO o/p continues even if the i/p disappears for a while  $\rightarrow$  used in clock recovery, freq. synthesis, FM demod.

## Mathematical analysis of PLL

- consider the following circuit

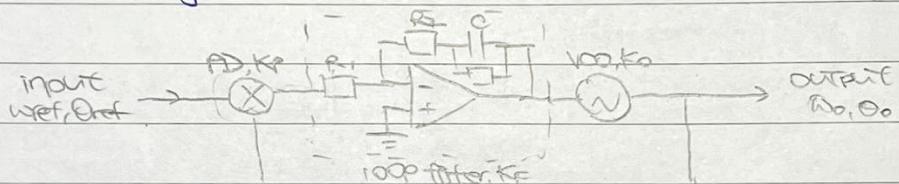

We implicitly assume the oscillating terms  $\theta_{ref}, \theta_o$  both oscillate at the same freq.  $w$ .

$$\theta_o = e^{j(\omega t + \theta)} \quad \theta_{ref} = e^{j\omega t}$$

- PD  $V_1 = K_p(\theta - \theta_{ref}) \quad [1]$

VCO  $w_o = K_v V_2 \rightarrow j\omega \theta_o = K_v V_2 \quad [2]$

Loop filter  $\frac{V_2}{V_1} = -\frac{R_2 + j\omega C_2}{R_1} \rightarrow V_2 = -V_1 \left( \frac{R_2}{R_1} + j\omega C_2 \right) \quad [3]$

- sub [1], [2] into [3],  $\frac{j\omega \theta_o}{K_v} = K_p(\theta - \theta_{ref}) \left( \frac{R_2}{R_1} + j\omega C_2 \right)$

$$\theta_o \left[ \frac{j\omega}{K_v} + K_p \left( \frac{R_2}{R_1} + j\omega C_2 \right) \right] = \theta_{ref} \left[ K_p \left( \frac{R_2}{R_1} + j\omega C_2 \right) \right]$$

$$\theta_o \left[ -\omega^2 \frac{C_2 R_1}{K_v R_0} + j\omega C_2 R_2 + 1 \right] = \theta_{ref} \left[ j\omega C_2 R_2 + 1 \right].$$

- Converting into std form using  $\omega_n^2 = \frac{K_v K_o}{C_2 R_1}$  and  $\zeta = \frac{\omega_n C_2 R_2}{2}$ ,

$$\theta_o \left[ \frac{-\omega^2}{\omega_n^2} + 2\zeta \frac{j\omega}{\omega_n} + 1 \right] = \theta_{ref} \left[ 2\zeta \frac{j\omega}{\omega_n} + 1 \right]$$

Since  $\dot{\theta}_{ref} = j\omega \theta_{ref}$ ,  $\ddot{\theta}_o = j\omega \dot{\theta}_o$ ,  $\ddot{\theta}_o = -\omega^2 \theta_o$ , we have a 2nd order ODE

$$\frac{\ddot{\theta}_o}{\omega_n^2} + \frac{2\zeta \dot{\theta}_o}{\omega_n} + \theta_o = \frac{2\zeta \dot{\theta}_{ref}}{\omega_n} + \theta_{ref}$$


(Mechanics of P12 case c):  $\frac{\ddot{x}}{\omega_n^2} + \frac{2\zeta}{\omega_n} x + y = \frac{2\zeta \dot{x}}{\omega_n} + x$

- \*  $\omega$  is neither the i/p signal  $w_{ref}$  nor the VCO freq.  $w_o$ , but rather the variation b/wn the two once the loop is locked (a rate of change of freq.)
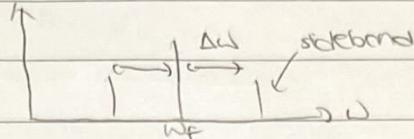
# For Personal Use Only -bkwk2

Phase locking of PLL.

- When there is a diff. in freq. b/w the i/p and o/p, the PD produces a component at this difference freq. (beat freq). Some of this gets through the filter to modulate the VCO and give IF sidebands in the o/p spectrum.




- One of the sidebands is the same as the ref. freq.  $\rightarrow$  PD gives DC component that steers the VCO freq. in the dir. to match the i/p.
- For  $S \approx 1$ , the time req. for locking is approximately given by

$$t \propto \frac{4\Delta\omega^2}{B^2}$$

where  $\Delta\omega$  is the initial freq. diff. and  $B$  is the loop BW, given by  $B = K_p K_v K_f$ .  
(If  $t$  is large up, achieving a locked phase is unlikely).

Frequency synthesis using PLLs.

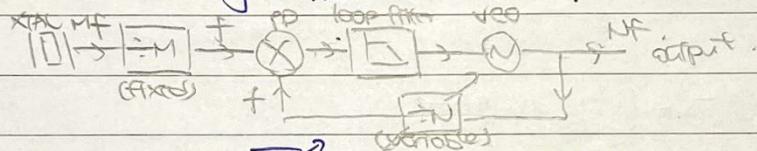- By introducing digital dividers, we can make a freq. synthesiser wrt PLLs.  
(divider circuits implemented using counters and MCUs).




where  $\boxed{1/M}$  is a fixed divider and  $\boxed{P/N}$  is a programmable divider

- By changing the division ratio  $N$ , the VCO can be made to run at diff. multiples of the local comparison freq.  $f$   $\rightarrow$  step freq. is equal to the local comparison freq.
- A crystal oscillator is usually used as the ref. oscillator, w/ typical freq.  $f_{ref} = 10 \text{ MHz}$ . This is too large a step size for most RF applications  $\rightarrow$  use fixed freq. divider  $\boxed{1/M}$

FM demodulation using PLLs.

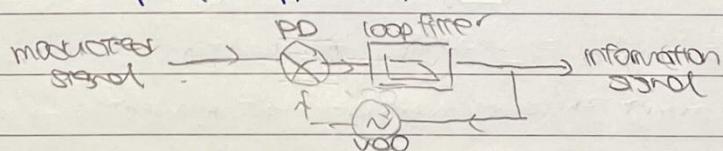- By taking the o/p at the loop filter o/p, (VCO i/p), the PLL acts as a FM demodulator.




- When the modulated signal has high freq., we expect the information signal (VCO o/p) to be high (since the VCO should give an o/p of high freq. to match the i/p), and vice versa.  
 $\rightarrow$  FM demodulation.

# For Personal Use Only -bkwk2


## Demodulation circuits

### AM demodulation

#### ① Simple diode circuit

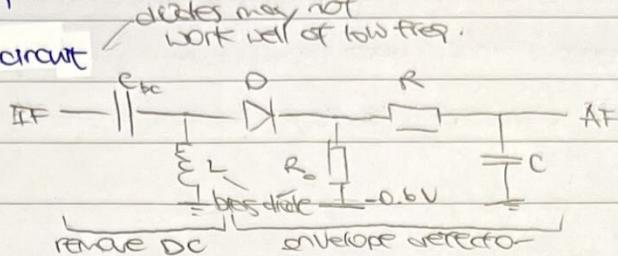


#### ② Active rectifier

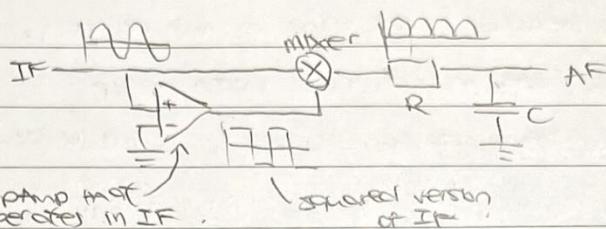


### FM demodulation

#### ① PLL (refer to previous section)

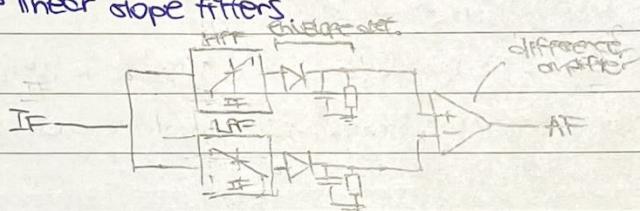
#### ② Matched inverse linear slope filters



#### ③ Time delay and mixer

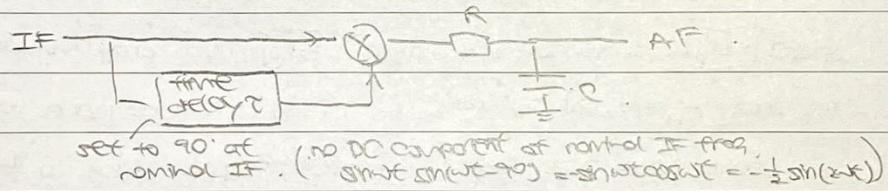
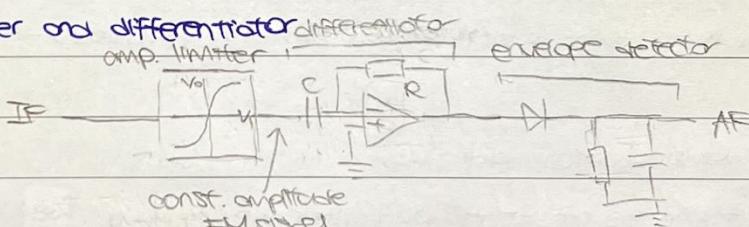
#### ④ Amplitude limiter and differentiator



$$\frac{d}{dt}[\sin(\omega t)] = \omega \cos(\omega t) \rightarrow \text{amplitude modulated}$$

Imperfect FM signal may have amplitude variation  $\rightarrow$  pass through as noise  $\rightarrow$  use limiter.

### Transmission lines and impedance matching

Equations for transmission lines and free space waves

- key eqns for t-lines and free space waves are as follows:

	Transmission lines	Free space waves
wave velocity	$v = \frac{1}{\sqrt{\mu_0 \epsilon_0}}$	$c_0 = \frac{1}{\sqrt{\mu_0 \epsilon_0}} = 3 \times 10^8 \text{ m s}^{-1}$
wave length	$\lambda = \frac{c}{f}$	$\lambda = \frac{c_0}{f}$
characteristic impedance	$z_0 = \sqrt{\frac{\mu_0}{\epsilon_0}}$	$\eta_0 = \sqrt{\frac{\mu_0}{\epsilon_0}} = 120\pi$
phase constant	$\beta = \frac{2\pi}{\lambda}$	$\beta = \frac{2\pi}{\lambda}$
voltage/field reflection coeff.	$\rho = \frac{z_L - z_0}{z_L + z_0}$	$\rho = \frac{1 - \eta_0}{1 + \eta_0}$
power reflection coeff.	$P = \rho^2$	$P = \rho^2$


### Controlled impedance transmission lines.

- For a coaxial cable w/ inner/outer radius  $a, b$ , w/ dielectric of rel. permittivity  $\epsilon_r$ ,

$$C_L = \frac{2\pi \epsilon_0 \epsilon_r}{\ln(b/a)} \quad v = \frac{1}{\sqrt{\mu_0 \epsilon_0}} = \frac{1}{\sqrt{\mu_0 \epsilon_r}} \\ \rightarrow z_0 = \sqrt{\frac{\mu_0}{C_L}} = \frac{1}{v C_L} = \frac{\sqrt{\mu_0 \epsilon_0 \epsilon_r} \ln(b/a)}{2\pi \epsilon_0 \epsilon_r} = \sqrt{\frac{\mu_0}{\epsilon_r} \frac{1}{\epsilon_r} \frac{\ln(b/a)}{2\pi}} = \frac{60}{\sqrt{\epsilon_r}} \ln(b/a) \quad [\sqrt{\frac{\mu_0}{\epsilon_0}} = 120\pi]$$


- Dimensions of the coaxial cable ( $a, b$ ) can be chosen to give the desired  $z_0$  (e.g. 50Ω, 75Ω)

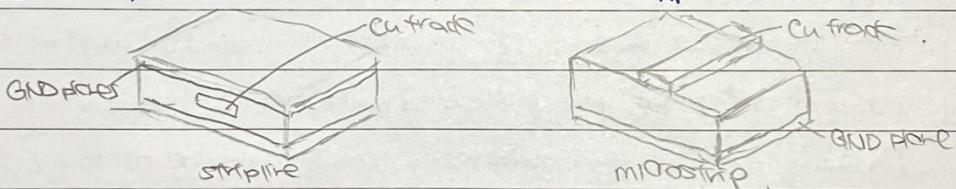- For PCB tracks, we can use the stripline or microstrip configuration



↳ stripline: lower loss, connection via top layer  
↳ microstrip: easy connections/inspection,

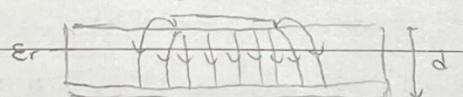- We can model a microstrip line as follows:



The capacitance per unit length of line may be estimated by

$$C_L = \frac{w_{eff} \epsilon_0 \epsilon_r}{d} = \frac{(w+2d) \epsilon_0 \epsilon_r}{d}$$

where we approx  $w_{eff} = w+2d$  to account for the fringing field lines (edge effects)

$$\rightarrow z_0 = \sqrt{\frac{\mu_0}{C_L}} = \frac{1}{v C_L} = \frac{\sqrt{\mu_0 \epsilon_r d}}{(w+2d) \epsilon_0 \epsilon_r} = \sqrt{\frac{\mu_0}{\epsilon_r} \frac{1}{\epsilon_r} \frac{d}{w+2d}} = \frac{120\pi}{\sqrt{\epsilon_r}} \frac{d}{w+2d} \quad [\sqrt{\frac{\mu_0}{\epsilon_0}} = 120\pi]$$

- dimensions of the microstrip ( $d, w$ ) can be chosen to give the desired  $z_0$  (e.g. 50Ω, 75Ω).

→ If  $w < 0$ , then the desired  $z_0$  is impossible to achieve w/ that particular material ( $\epsilon_r$ ).  
and dielectric thickness  $d$ .

# For Personal Use Only -bkwk2

## Impedance matching using transmission line


- At high freq, if connection length is a large fraction of  $\lambda$  ( $\sim \lambda/16$ ), we should consider the connection as a transmission line if distortions from reflections/phase delays are to be avoided.
  - The i/p impedance  $Z_{in}$  for a length of  $\ell$ -line (of characteristic impedance  $z_0$ ) terminated w/ a load impedance  $z_L$  is given by
- $$Z_{in} = z_0 \frac{z_L + z_0 j \tan(\beta L)}{z_0 + z_L j \tan(\beta L)}$$
- 
- It is difficult to find req. values of  $\beta L$  to provide a particular  $Z_{in}$   $\rightarrow$  we can solve this graphically using a Smith chart.

## Smith chart.


- By const. of energy, for fixed  $z_0$ , then  $|T| = \rho \leq 1$ , i.e unit circle on Smith chart
- Complex impedance is represented on the Smith chart as normalised impedance  $\bar{z}$
- so that the same chart can be used at diff. reference impedances  $z_0$ ,  $\bar{z} = \frac{z}{z_0}$ .
- when  $\bar{z} = z_0$ ,  $T = 0$ , so the prime centre represents  $\bar{z} = 1 + 0j$
- Lines of const. resistances form a set of circles all converging at  $\bar{r} = 1$  (open circuit pt.)  
Lines of const. reactances form a set of arcs away from  $\bar{r} = 1$  (open circuit pt.)
- Lines of const resistances and reactances meet at right angles.
- There are multiple axes and the outside of the chart for phase of reflection, electrical length.
- For a particular pt. radially scaled parameters can be found at the bottom scale.
- Adding a  $\ell$ -line (towards generator/source) would be rotating CW on the Smith chart  
(Full rotation ( $360^\circ$ )  $\leftrightarrow \lambda/2$ , scale accordingly for other lengths of tailine).
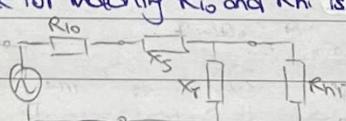
## Impedance matching network (L-network)

- A simple impedance matching network for matching  $R_{in}$  and  $R_{out}$  is as follows.



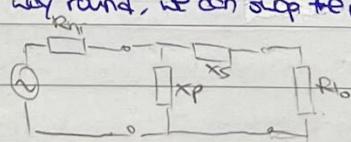If  $R_{in}$  and  $R_{out}$  are swapped the other way round, we can swap the position of  $X_S$  and  $X_P$




Alternatively, matching must work in both directions, we can simply consider the first circuit.  
depends on LPF or HPF

- $X_P, X_S$  are given by  $\omega L$  or  $1/\omega C$  as appropriate, but we cannot have both  $X_P/X_S$  as inductors/capacitors. (LPF:  $X_S = \omega L$ ,  $X_P = \frac{1}{\omega C}$ ; HPF:  $X_S = -\frac{1}{\omega C}$ ,  $X_P = \omega L$ )
- The values of  $\omega$ ,  $C$ ,  $L$  can be solved by calculation or using the Smith chart.

# For Personal Use Only -bkwk2
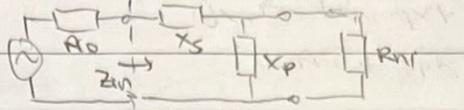
## ① Calculation.

- Consider the first circuit. (since arranging  $R_{hi}$  and  $R_{lo}$  in both ways yield the same result)



$$Z_{in} = Z_S + \frac{R_{hi} \cdot Z_P}{R_{hi} + Z_P} = Z_S + \frac{jX_P R_{hi}}{R_{hi} + jX_P} = jX_S + \frac{jX_P R_{hi}}{R_{hi}^2 + X_P^2} = jX_S + \frac{jX_P R_{hi}^2 + X_P^2 R_{hi}}{R_{hi}^2 + X_P^2}$$

If we choose  $X_S$  s.t.  $\text{Im}[Z_{in}] = 0$ , and we req.  $\text{Re}[Z_{in}] = R_{lo}$ , then

$$R_{lo} = \frac{X_P^2 R_{hi}}{R_{hi}^2 + X_P^2} \rightarrow R_{lo}(R_{hi}^2 + X_P^2) = X_P^2 R_{hi} \rightarrow X_P^2(R_{hi} - R_{lo}) = R_{lo} R_{hi}^2 \rightarrow X_P = \frac{R_{hi}^2}{Q}$$

$$X_S = -\frac{X_P R_{hi}^2}{R_{hi}^2 + X_P^2} = -\frac{R_{hi}/Q \cdot R_{hi}^2}{R_{hi}^2 + R_{hi}^2/Q^2} = -\frac{R_{hi}/Q}{1 + 1/Q^2} = -\frac{R_{hi}Q}{Q^2 + 1} = -\frac{R_{hi}Q}{R_{hi}/R_{lo}} = -QR_{lo}$$

where we define the filter Q-factor  $Q = \sqrt{\frac{R_{hi} - R_{lo}}{R_{lo}}} = \sqrt{\frac{R_{hi}}{R_{lo}} - 1}$ . [so  $Q = \frac{R_{hi}}{X_P} = \frac{|X_S|}{R_{lo}} = \sqrt{\frac{R_{hi}}{R_{lo}} - 1}$ ]

- Note that the effective Q-factor  $Q_f$  is half the filter Q-factor Q,

$$Q_f = \frac{Q}{2}$$

- To produce a filter w/ a sharp response (high Q), we connect a pair of matching networks connected back-to-back w/ a hi-lo-hi impedance transition. The half power bandwidth  $B$  is given by

$$B = \frac{f_0}{Q} = \frac{f_0}{Q_f}$$


- To obtain a broadband match, a series of matching networks can be cascaded w/ gradually changing intermediate impedances (low Q).

+ Note we can obtain expressions for  $\frac{R_{hi}}{R_{lo}}$  or  $w^2$  using  $\frac{R_{hi}}{X_P} = \frac{|X_S|}{R_{lo}}$  and  $\frac{R_{hi}}{X_P} = \frac{R_{hi}}{R_{lo}} - 1$ .

+ If the load has a resistive component, it can be cancelled out by adding an additional series resistance.
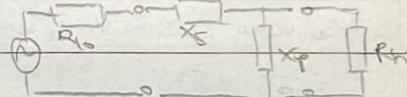
## ② Smith chart

- We can always find an equivalent circuit in the form of the first circuit.



- We can find the req. C, L values using a Smith chart as follows:

↳ 1) Plot the normalized load impedance [pt A]

↳ 2) Plot the reciprocal of pt A and add the admittance  $\frac{1}{Z_P}$  (CCW for inductor, CW for capacitor) by drawing on arc w/ const. conductance (real part). [pt. B]

↳ 3) Find the pt. on the arc s.t. when reflected dot the primal centre back on the unity resistance circle.

(Found by drawing circles centred at  $3/4$  and finding its intersection w/ the arc) [pt. C]


↳ 4) Add the impedance  $Z_S$  (CW for inductor, CCW for capacitor) by completing the path from pt C to the primal centre along the unity resistance circle.

↳ 5) Find  $X_P, X_S$  values by finding the reactive component of pt. B, C. → Find C, L

- Note that taking the reciprocal of a pt. on the Smith chart is simply rotating and the primal centre by  $180^\circ$  or reflecting abt. the primal centre.
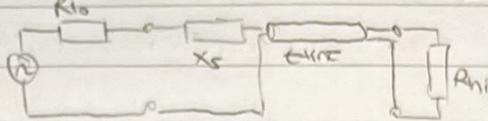
# For Personal Use Only -bkwk2

- Actually, we can replace  $X_P$  w/ a t-line connected in series for impedance matching.



- We can find the req. C/L value and length of t-line using a Smith chart as follows:

↳ 1) Plot the normalised load impedance, [pt A]

↳ 2) Add a length of t-line by rotating CW s.t. it intersects w/ the unity resistance circle [pt B]

↳ 3) Add the impedance  $Z_S$  (CW for inductor, CCW for capacitor) by completing the path from pt. B to the prime centre along the unity resistance circle.

↳ 4) Find  $X_S$  value by finding the reactive component of pt. B  $\rightarrow$  Find C/L.

Find length of t-line by considering the change in wavelength (forward generator) from pt A to pt.B

(We find wavelength  $\lambda$  using  $\lambda = \frac{V}{f}$ , where  $V = \sqrt{Z_0 C_L}$  and  $Z_0 = \sqrt{\frac{L_C}{C_L}}$ )


- We replace  $X_P$  w/ a t-line when we want to avoid using inductors, which are rel expensive.

(so we would use a capacitor for  $X_S$ ).

## $S$ and $Z$ parameters - two port networks

- We can characterise the behaviour of two-port networks using Impedance ( $Z$ ) or scattering ( $S$ ) parameters.

### ① Z-parameters.

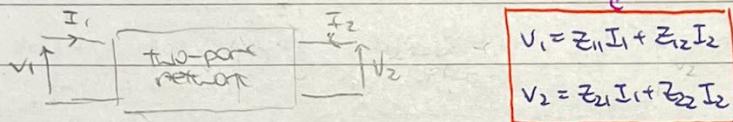


$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$

↳ Find  $Z_{11}$  by setting  $I_2 = 0$  and considering the impedance at port 1

Find  $Z_{21}$  by setting  $I_1 = 0$  and finding the voltage at port 2 rel-to port 1 (e.g. potential divider)

similar steps for  $Z_{12}, Z_{22}$

### ② S-parameters.

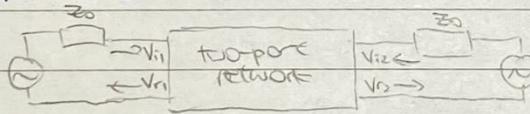

$$\begin{aligned} S_{11} &= \frac{V_{1r1}}{V_{1i1}} & S_{12} &= \frac{V_{1r2}}{V_{1i2}} \\ S_{21} &= \frac{V_{2r1}}{V_{2i1}} & S_{22} &= \frac{V_{2r2}}{V_{2i2}} \end{aligned}$$

↳ For an ideal amplifier of linear gain G w/ load applied, (i)  $S_{11} = S_{22} = 0$  (no reflection at  $V_P$ /or  $V_P$ )

(ii)  $S_{21} = G$  and (iii)  $S_{12} = 0$  (no coupling back from the load to the  $V_P$ ).

↳ We can match impedances using S-parameters by considering  $S_{11}/S_{22}$ . This can be done by shifting the reflection coefficient  $S_{11}/S_{22}$  (reflection coeff magnitude + angle) and match as before

- At low freq., it is often useful to consider Z-parameters as they can be measured easily using open and short circuits on the ports while measuring voltage/current applied.

- At high freq., it is not so easy to make good open and short circuits due to reflections, which may even destroy the DUT, so we use S-parameters instead.

# For Personal Use Only -bkwk2

## Antennas

Terms and definitions in antenna efficiency.

- The radiation resistance of an antenna  $R_r$  is defined as

$$P_r = \frac{1}{2} I^2 R_r = I_{max}^2 R_r \quad \text{where } P_r \text{ is the radiated power}$$

- The radiation efficiency of an antenna  $\eta$  is defined as

$$\eta = \frac{P_r}{P_{in}} \quad \text{where } P_{in} = \frac{1}{2} I^2 (R_r + R_{ohmic}) = I_{max}^2 (R_r + R_{ohmic})$$

- The Poynting vector  $\bar{N} = \vec{E} \times \vec{H}$  has magnitude equal to the instantaneous power density (power per unit area), and has an average value given by  $|\bar{N}|$

$$|\bar{N}| = \frac{|E||H|}{2} = E_{max} H_{max}$$

- The gain of an antenna  $G$  is defined as

$$G = \frac{\text{max. power density}}{\text{power density for ideal isotropic antenna}} = \frac{|\bar{N}|_{max}}{|\bar{N}|_{iso}} \quad \text{where } |\bar{N}|_{iso} = \frac{P_r}{4\pi r^2}$$

- The directivity of an antenna  $D$  is defined as

$$D = \frac{\text{max. power density}}{\text{power density for lossy isotropic antenna}} = \frac{|\bar{N}|_{max}}{P_r/4\pi r^2} = \frac{|\bar{N}|_{max}}{|\bar{N}|_{iso}\eta} = \frac{G}{\eta}$$

- The effective area / aperture of an antenna  $A_e$  is defined as

$$A_e = \frac{P_{abs}}{|\bar{N}|} \quad \text{where } P_{abs} \text{ is the power delivered into a matched load by the antenna.}$$

- The beam angle  $d\phi$  can be related to the directivity  $D$ .

$$D = \frac{P_r/\pi(r d\phi)^2}{P_r/4\pi r^2} = \frac{4}{(d\phi)^2}$$

- The Friis transmission eqn. (Antenna eqn) relates the ratio of received/transmitted radiative power  $\frac{P_{r,r}}{P_{r,t}}$

to the effective apertures  $A_{e,r}, A_{e,t}$  or the gains  $G_r, G_t$  of the two antennas.

$$\frac{P_{r,r}}{P_{r,t}} = \frac{A_{e,r} A_{e,t}}{\pi^2 \lambda^2} = G_r G_t \left(\frac{\lambda}{4\pi r}\right)^2$$

since  $A_{e,r} = \frac{P_{r,r}}{G_t P_{r,t}/4\pi r^2} = \frac{P_{r,r}}{P_{r,t}} \frac{4\pi r^2}{G_t}$  and  $A_{e,t} = \frac{P_{r,r}}{G_r P_{r,t}/4\pi r^2} = \frac{P_{r,r}}{P_{r,t}} \frac{4\pi r^2}{G_r}$

The Antenna eqn. is usually written in the form

$$G_r = \frac{4\pi A_{e,r}}{\lambda^2}$$

↳ usually set  $A_{e,r}$  to  $\lambda/2^2$

- The skin depth of a conductor  $\delta$  is given by

useful for finding  
 $R_{ohmic}$

$$\delta = \sqrt{\frac{2}{\omega \mu \sigma}}$$

## Size of antennas



- For efficient radiation, the antenna needs to be comparable to a good fraction of a wavelength in dimension.

- (i) Consider a small loop driven by an oscillating current  $\rightarrow$  all parts of the circuit carry a current which is inphase.

At far-field, any current segment  $\propto 1/E$ , it tends to have nearby in antiphase  $\rightarrow$  cancels out  $\rightarrow$  no radiate energy.

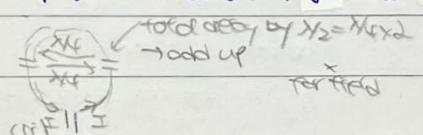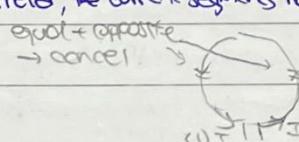- (ii) consider a larger loop driven by an oscillating current  $\propto I$ . there is a phase change in the loop ( $\pi/4$  across).


At far field, the current segments now add up due to the static phase shift in current  $\rightarrow$  radiate energy.


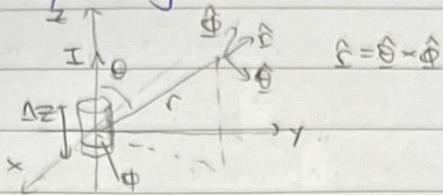
# For Personal Use Only -bkwk2

The ideal dipole

- Consider the ideal dipole - a tiny radiating current element.



A differential patch  $dS$  is given by  $dS = r^2 \sin\theta d\phi d\theta \hat{f}$

- It can be shown using Maxwell's eqns that the far field  $E$  and  $H$  are given by

$$E = \frac{I \Delta z}{4\pi r} j \omega m e^{-jkr} \sin\theta \hat{e}_r \quad H = \frac{I \Delta z}{4\pi r} j \beta e^{-jkr} \sin\theta \hat{e}_\theta$$

We can find the power radiated  $P_r$  by integrating  $|\bar{N}| = \frac{1}{2} \bar{E} \times \bar{H}^*$  over a complete sphere.

$$P_r = \frac{1}{2} \int \int \int |\bar{N}|^2 dS = \frac{1}{2} \left( \frac{I \Delta z}{4\pi} \right)^2 \omega M \beta \int \int \int \frac{1}{r^2} (r^2 \sin\theta) d\phi d\theta = \frac{1}{2} \left( \frac{I \Delta z}{4\pi} \right)^2 \omega M \beta \int_0^{2\pi} d\phi \int_0^\pi \sin^2\theta d\theta$$

Noting that  $\int_0^\pi \sin^2\theta d\theta = \int_0^\pi (3\sin\theta - \sin 3\theta) d\theta = \frac{\pi}{3}$ , we have

$$P_r = \frac{1}{2} \left( \frac{I \Delta z}{4\pi} \right)^2 \omega M \beta (2\pi) \left( \frac{\pi}{3} \right) = 40\pi^2 I^2 \left( \frac{\Delta z}{\lambda} \right)^2$$

(where we used  $\omega = \frac{2\pi c}{\lambda}$ ,  $\beta = \frac{2\pi}{\lambda}$ ,  $c_0 = 3 \times 10^8 \text{ m/s}$ ,  $M = 4\pi \times 10^7 \text{ Hm}^{-1}$ ).

- Since the radiation resistance  $R_r$  is defined as  $P_r = \frac{1}{2} I^2 R_r$ , for the ideal dipole

$$R_r = 80\pi^2 \left( \frac{\Delta z}{\lambda} \right)^2$$

-  $E$  and  $H$  are max. when  $\theta = 90^\circ$ , and the corresponding peak radiated power density at  $r_\text{apex}$  is

$$\text{note } \eta_0 = \frac{|E|}{|E_0|} = \sqrt{\frac{M}{\epsilon_0}} = 20\pi \rightarrow |\bar{N}|_{\text{peak}} = \frac{1}{2} |\bar{E}| |\bar{H}| = \frac{1}{2} \frac{|E|^2}{\eta_0} = \frac{1}{2} \left( \frac{I \Delta z}{4\pi r} \omega M \right)^2 = 15\pi^2 \frac{1}{r^2} I^2 \left( \frac{\Delta z}{\lambda} \right)^2$$

The power density for an ideal isotropic antenna  $|\bar{N}|_{\text{iso}}$  is given by


$$|\bar{N}|_{\text{iso}} = \frac{P_r}{4\pi r^2} = \frac{Y_2^2 R_r}{4\pi r^2} = \frac{I^2}{8\pi r^2} (80\pi^2 \left( \frac{\Delta z}{\lambda} \right)^2) = 10\pi^2 I^2 \left( \frac{\Delta z}{\lambda} \right)^2$$

Therefore the gain  $G$  and directivity  $D$  are given by

$$D = G = 1.5 \quad \checkmark \text{ since } \eta = 1 \text{ for ideal dipole}$$

- In practice, it is not possible to make an ideal dipole, but any antenna can be made up by

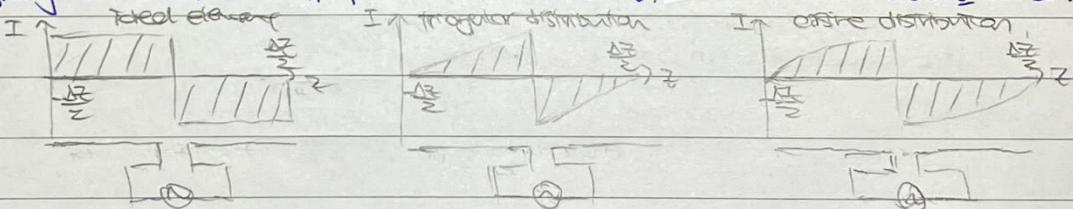integrating the ideal dipole w/ appropriate current distributions, to calculate the far field  $E$  and  $H$ .



- The simplest example is a triangular current distribution, w/ a central peak and dropping to 0 at the ends.

Since  $\text{tria}(\Delta z)^2$ ,  $R_r$  for the triangular current distribution is  $(\frac{1}{2})^2 \times \text{tria} R_r$  for the ideal element.

- For  $\Delta z \sim \frac{\lambda}{2}$ , the triangular current distribution becomes closer to a cosine current distribution,

and the corresponding  $R_r$  is  $R_r = 30\pi^2 \left( \frac{\Delta z}{\lambda} \right)^2$


- There is actually a series inductive reactance  $\rightarrow$  trim antenna length slightly  $\rightarrow$  introduce some capacitance to cancel out. (such parasitic reactions are small for large  $R_r$ , i.e. large antennas)

- Smaller antennas have low  $R_r$ , and thus low efficiency  $\eta$  (since  $\eta = \frac{P_r}{P_r + P_{loss}}$ )  $\rightarrow$  poor at radiating, but effective for receiving.  $\rightarrow$  use larger antenna for transmitting.


# For Personal Use Only -bkwk2
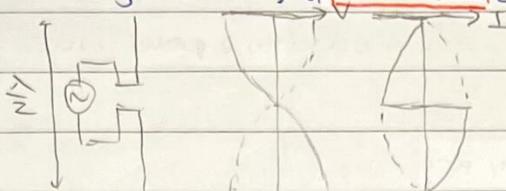
## Half-wave dipole

- The half-wave dipole is  $\frac{\lambda}{2}$  m length and supports a resonant standing wave along it, giving a cosine current distribution and a sine voltage distribution, w/  $R_r = \rho \sigma r^2 \left(\frac{\lambda}{2}\right)^2$  and  $D \approx 1.5$




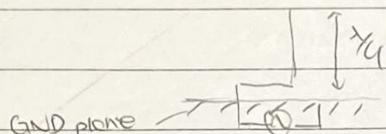- We can also consider a monopole above a conductive GND plane — a reflection of the monopole gives the same profile as the dipole (radiates half the space → D doubled, Rr halved)


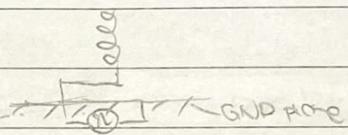
## Helical antenna.


- The size of a half-wave dipole can still be large → helical antenna considered as a more compact version where the length of conductor is coiled up into a spiral.




- The helical antenna is less efficient and its structure is not necessarily resonant, but it radiates circularly polarised EM waves. (a pair of linearly polarised EM waves orthogonal and 90° out of phase),  $\nwarrow$  will receive signals even if receiver antenna misaligned.
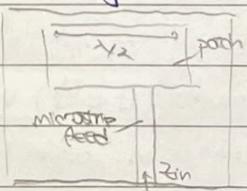
## Microstrip patch antenna.

- A length of microstrip (patch) can be made to resonate as a halfwave dipole, supporting a standing wave end to end, excited by an off-centre microstrip feed.
- The microstrip feed usually has characteristic impedance  $Z_0$  and is off-centre of the patch so it is impedance-matched and can excite the standing wave easier. (hard to do so at the node).



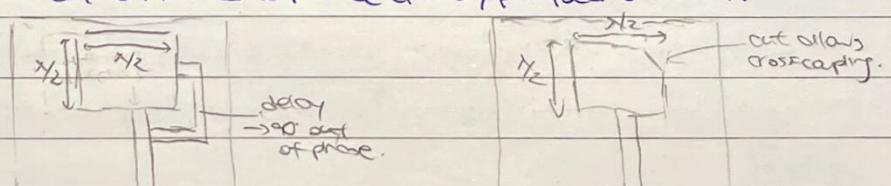- If the substrate has a high rel. permittivity ε\_r, the patch can be very small ( $V_{eff} \frac{1}{\epsilon_r}$ ,  $\lambda_{eff} \propto \sqrt{\frac{1}{\epsilon_r}}$  so  $\lambda \propto \frac{1}{\sqrt{\epsilon_r}}$ ).
- The microstrip patch can be modified to produce circularly polarised EM waves.




# For Personal Use Only -bkwk2

Power dividers, directional couplers and circulators.

Resistor network

- Consider the following resistor network, where each port presents a characteristic impedance  $Z_0$ .

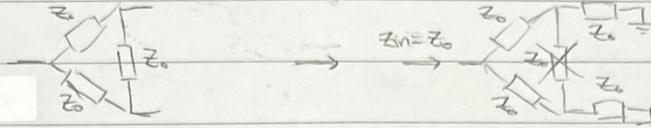Viewing from any port is equivalent to two parallel branches of two series  $Z_0$




- Half the power is dissipated in the internal resistors and power is split equally across all ports,

so each o/p port has  $\frac{1}{4} \times$  power of i/p port  $\rightarrow$  6dB splitter.

- This configuration is freq. independent.

Wilkinson coupler

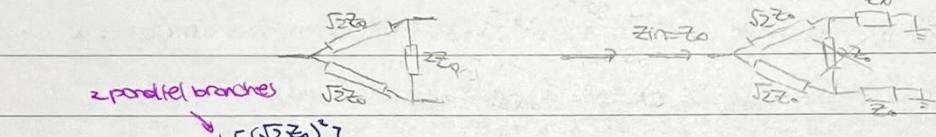- The Wilkinson coupler comprises a pair of uncoupled lines, each  $\frac{1}{4}$  long w/ characteristic impedance  $\sqrt{2}Z_0$ .




$$\text{Note that } Z_{in} = \frac{1}{2} \left[ \frac{(Z_0)^2}{Z_0 + \sqrt{2}Z_0} \right] = Z_0 \rightarrow \text{impedance matched}$$

- Power in P1 is split equally to P2 and P3, so each o/p port has  $\frac{1}{2} \times$  power of i/p port  $\rightarrow$  3dB splitter.

- Power in P2/P3 is only coupled to P1, but not P3/P2, since the contributions via the resistor and  $\lambda/2 = \lambda/4 + \lambda/4$  line lengths are in antiphase and cancel  $\rightarrow$  good isolation ( $\sim 20\text{dB}$ ) b/w P2, P3.

Hybrid ring coupler (refracte coupler)

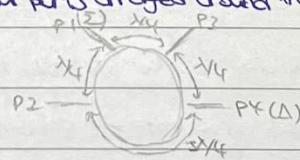- The hybrid ring coupler is a four-port 3dB directional coupler consisting of a  $3\frac{1}{2}$  ring of t-line of characteristic impedance  $\sqrt{2}Z_0$ , w/ four ports arranged around the ring.



- Power in P1 splits and travels both ways around the ring.

$\hookrightarrow$  P2/P3: signals arrive in phase and add ( $\frac{\lambda}{4}$  vs  $\frac{3\lambda}{4}$ )

$\hookrightarrow$  P4: signals arrive in anti-phase and cancel ( $\frac{\lambda}{2}$  vs  $\lambda$ )

$\rightarrow$  Power in P1 is split equally to P2 and P3, so each o/p port has  $\frac{1}{2} \times$  power of i/p port  $\rightarrow$  3dB splitter.

- If power is directed into P2 and P3, then


$\hookrightarrow$  P1: signals arrive in phase and add ( $\lambda/4$  vs  $\frac{\lambda}{4}$ )  $\rightarrow$  sum signal ( $\Sigma$ )

$\hookrightarrow$  P4: signals arrive in anti-phase and cancel ( $\frac{3\lambda}{4}$  vs  $\frac{\lambda}{4}$ )  $\rightarrow$  difference signal ( $\Delta$ ).

# For Personal Use Only -bkwk2
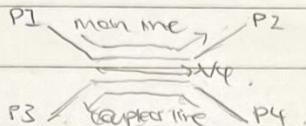
## Directional coupler

- Instead of splitting the power evenly, the directional coupler can just tap off a fraction of the power being directed into a system (e.g. power meter to monitor signal reflection or an antenna).
- This can be achieved by running parallel microstrip lines close to each other for a short length. The fields couple across and tap off a fraction of the power ( $\downarrow$  distance  $\rightarrow$  coupling  $\rightarrow$   $\uparrow$  power tapped off).




- Most of the power input to P1 is routed through to P2, but a fraction is tapped off to P3 (but none to P4), and vice versa for power input to P2.
- Using signal detectors at P3, P4, we can monitor how much power is going to P2 / reflected back.

## Circulators

- Circulators are useful when we req. nonreciprocal operation (e.g. unidirectional routing of a signal).


All power into P1 goes to P2, all power into P2 goes to P3 etc..

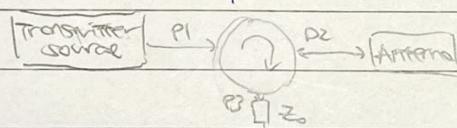- If P3 is simply a matched load, then we have an isolator — a device which protects the transmitter source from reflection (which could destroy it).



The isolator only routes power from P1 to P2, but not the other way around.

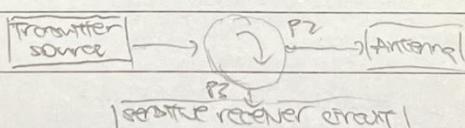
- The circulator could also protect sensitive receiver circuitry from power-transmitted signals, which is also connected to the same antenna.



Circulators are limited in BW and typically have fairly low isolation of ~20dB.
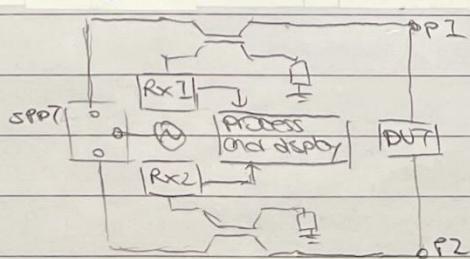
## Vector Network Analyser (VNA)

- A VNA can separate forward and reflected waves  $\rightarrow$  we can measure S-parameters.
- The circuit/block diagram for the VNA is as follows:



- When the isolator is applied to P1, signal at Rx1 gives  $S_{11}$  and signal at Rx2 gives  $S_{21}$ .